

2B 2-26-14

## QUIZ 19 CH. 19

## QUIZ 19

SAMPLE EXAM 1 SP'11

SAMPLE EXAM2 SP'12

SELECTED DISCUSSIONS TO exercises/problems BELOW.

YOU ARE RESPONSIBLE FOR ALL PROBLEMS EVEN THE ONES WITHOUT DISCUSSIONS, WHICH ARE DESIGNED TO HELP YOU DO RELATED EXERCISES.

CH. 19 MULTIPLE CHOICE TBA - Exercise/problems 2, 5, 9, 10, 15, 21, 26, 27, 40, 42, 46, 49, 52, 57, 64, 65, 66

TURN IN: 2 (try 5), 10 (try 9), 15, 21, 26, 27, 40 (try 42), 52 (try 49 and 46), 57, 65 (try 64 and 66)

\* DISCUSSIONS PROVIDED.

## DISCUSSIONS

2.  $Q = I \cdot t$ .

10.  $R = (\text{Cu resistivity}) \cdot L/A$  and  $R' = (\text{Al resistivity}) \cdot L/A'$ .  $R/R' = (\text{Cu resistivity}) \cdot A' / [(\text{Al resistivity}) \cdot A] =$

$(\text{Cu resistivity}) \cdot d'^2 / [(\text{Al resistivity}) \cdot d^2] = 1$ . Find  $d$  given  $d' = 3.26 \text{ mm}$ .

15. (a)  $I = 18.5 \text{ (A)} = |\text{change in } V|/R$ , where  $R = (\text{resistivity}) \cdot L/A$  at  $20.0$  degrees C. Find resistivity.

(b)  $17.2 \text{ (A)} = |\text{change in } V|/R'$ , where  $R' = (\text{resistivity}') \cdot L/A$ , where resistivity' = resistivity  $\cdot [1 + \alpha \cdot \text{change in temp}]$ ; change in temp =  $(92.0 - 20.0)$  degrees C and resistivity was found in part a. Find  $\alpha$ .

21.  $I = |\text{change in } V|/R$ , where  $R$  varies between  $1 \text{ k-ohm}$  and  $500 \text{ k-ohm}$ . Set  $R$  to the lowest value (when you are wet) and  $I = 5.0 \text{ mA}$  to find  $|\text{change in potential}|$ .

26.  $6.00 \text{ (V)} = I \cdot r + I \cdot R = I \cdot (r + R)$ . Find  $r$  given  $R$  and  $I$ .

27. Open circuit (switch open) means  $I = 0$ . Then the voltmeter would read the voltage difference across the battery only since there is no voltage drop across the resistors  $r$  and  $R$ . That battery voltage =  $3.08 \text{ (V)}$ . When switch is closed, use battery voltage to solve: battery voltage =  $I \cdot r + I \cdot R$  for  $r$  and  $R$ . Use  $2.97 \text{ (V)} = \text{battery voltage} - I \cdot r$ . Find  $r$  from the latter equation and solve for  $R$  in the former equation. Note:  $I = 1.65 \text{ (A)}$  when switch is closed.

40. (a)  $P = 540 \text{ (W)} = V^2/R$  (b)  $I = V/R$ , where  $V$  is the magnitude of the voltage drop across  $R$ . (c)  $P \cdot \text{time} \cdot 7.4 \text{ cents/KW-h} = \text{cost}$ . Note: time =  $1 \text{ h}$ . Convert  $P = 540 \text{ (W)}$  to  $(\text{kW}) = 0.540 \text{ (kW)}$ .

(d)  $P = V^2/R$ . We assume  $R$  is constant though we know it'll change as the temperature varies.

49. (a) See Test #1, Problem 3(Sp 12):  $1/R_p = 1/40.0 + 1/90.0$  so  $R_p = (40) \cdot (90) / (40 + 90)$  which you should simplify.

(b)  $I = 120 \text{ (V)} / R_p$

(c)  $I_{90} = 120 \text{ (V)} / 90$  and  $I_{40} = 120 \text{ (V)} / 40$ .

THESE  
COULD  
BE ON  
TEST 2

52. (a) Moving left to right on the bottom branch of circuit:  $1/R_{p1} = 1/3.00 + 1/6.00$  and  $1/R_{p2} = 1/12.0 + 1/4.00$ .

Find  $R_{p1} + R_{p2}$ .

(b) Now,  $60.0 \text{ (V)} = I * (R_{p1} + R_{p2})$ . Find  $I$ . Then find  $I * R_{p1}$  and  $I * R_{p2}$ .

From these latter two values you can find each of 4 currents:  $I_3 = I * R_{p1} / 3$ ,  $I_6 = I * R_{p1} / 6$ ,  $I_{12} = I * R_{p2} / 12$  and  $I_4 = I * R_{p2} / 4$ .

57. See example 11.

At top Node:  $I = I_{30} + I_{20}$ , where  $I$  flows through the  $10.0 \text{ (V)}$ -battery upward in the branch, and  $I_{30}$  and  $I_{20}$  flow downward in the branches for the  $30 \text{-ohm}$  and  $20.0 \text{ ohm resistor/}5.00 \text{ (V)- battery}$ , respectively.

You need two other equations from which to find  $I$ ,  $I_{30}$  &  $I_{20}$ . They are, using the law that the sum of the voltage drops around an internal loop of the circuit is zero: clockwise in the left loop,  $10.00 \text{ (V)} - I_{30} * (30 \text{ ohm}) = 0$  and

counterclockwise in the right loop,  $5.00 \text{ (V)} + I_{20} * (20 \text{ ohm}) - I_{30} * (30 \text{ ohm}) = 0$ .

Note the positive term  $I_{20} * (20 \text{ ohm})$  in the last equation due to the fact we are going counter clockwise in the right loop and thus *against* current  $I_{20}$ .

65. This is a very important problem which I will be sure to grade. It is an RC circuit from which we'll do a lab later this coming month.

(a) This is a charging process- $Q$  on the capacitor's positive plate grows according to the second of equations 19.17.

$Q = Q_m * (1 - e^{-t/RC})$ . Note:  $Q_m$  = maximum charge at the end of the process - when current  $I = 0$ .  $Q_m = C * V$ , where  $V = 60.0 \text{ (V)}$ . Note  $RC$  is easily computed from the given info. Plug in various times into the formula and you will notice  $Q$  increases with time  $t$ .

(b) Plug in various times  $t$  into the first of equations 19.17:  $I = I_0 * e^{-t/RC}$ . You will notice  $I$  decreases with time  $t$ .

(c) Make a sketch. We 'll examine detailed graphs in upcoming RC lab.