

# test 3 2B solutions (1)

1.

a.

$$A = \pi r^2 = (3.14)(0.03)^2 = 2.83 \times 10^{-3} \text{ m}^2$$


b.

$$|\mathcal{E}| = N \cdot A \frac{\Delta B}{\Delta t} = (1)(2.827 \times 10^{-3}) \cdot 10 = 2.83 \times 10^{-2} \text{ (V)} = 28.3 \text{ mV}$$

c.


$$I = \frac{|\mathcal{E}|}{R} = \frac{28.27 \times 10^{-3} \text{ (V)}}{40 \Omega} = 0.706 \times 10^{-3} = 0.706 \text{ mA}$$

d.

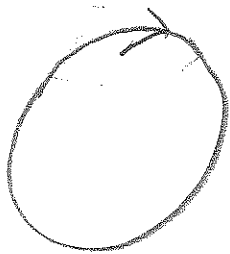

(test sheet below.)

e.

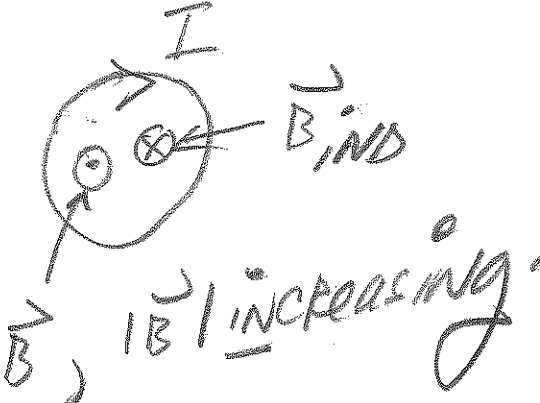

2.

a.

$$L = \frac{|\mathcal{E}|}{\frac{di}{dt}} = \frac{0.0160 \text{ (V)}}{0.1280 \text{ A/s}} = 0.125 \text{ H} = 125 \text{ mH}$$

b.

Left end higher; voltage induced opposes increase in I.

# Test 3 2B

(3.)

$$\frac{N_2}{N_1} = \frac{V_2}{V_1}$$

$$\frac{834}{275} = \frac{V_2}{25}$$

$$V_2 = \left(\frac{834}{275}\right) \cdot 25$$

$$= 76 \text{ (V)}$$

(b.) step up

(c.)

EXTRA  
credit discussion  
LATER:

ANSWER: 13.6  $\Omega$

(4.)

$$\frac{1}{2} C V_i^2 = U$$

$$= \frac{1}{2} 10 \times 10^{-6} (10)^2$$

$$= \frac{1}{2} (1000) \times 10^{-6}$$

$$= 500 \times 10^{-6}$$

$$= 0.500 \times 10^{-3} \text{ J}$$

$$= 0.500 \text{ mJ}$$

(b.)

$$\frac{1}{2} L (0.5)^2 = 0.500 \times 10^{-3}$$

$$L = \frac{1 \times 10^{-3}}{0.25}$$

$$L = 4 \times 10^{-3} \text{ H}$$

$$L = 4 \text{ mH}$$

$$Q = 0 \text{ when } I = I_m$$

(c.)

$$W = \frac{1}{\sqrt{LC}}$$

$$= \frac{1}{\sqrt{4 \times 10^{-3} \cdot 10^{-5}}} = \sqrt{0.25 \times 10^8}$$

$$= 0.5 \times 10^4 = 5 \times 10^3$$

$$= 5000 \text{ RAD/S}$$

(2)

test 3

(5.) a, b, c

$$Z = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

W (RAD/S)	$\omega L - \frac{1}{\omega C}$	MATH WORK:
1001	$403.45 \Omega$	$1001 \cdot (0.902) - \frac{1}{(1001)(2 \times 10^{-6})} = 403.45 \Omega$
751	$11.62 \Omega$	$751 \cdot (0.902) - \frac{1}{(751)(2 \times 10^{-6})} = 11.62 \Omega$
502	$-543 \Omega$	$502 \cdot (0.902) - \frac{1}{(502)(2 \times 10^{-6})} = -543 \Omega$

2 B

$$Z = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2} \quad (3)$$

1001

$$\sqrt{201^2 + 403.4^2}$$

$$= 450.7 \Omega$$

751

$$\sqrt{201^2 + 11.62^2}$$

$$= 201.34 \Omega$$

502

$$\sqrt{201^2 + (-543)^2}$$

$$= 579 \Omega$$

(d)

$$\frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(0.902)(2.01 \times 10^{-6})}} = 743.3 \frac{\text{RAD}}{\text{S}}$$

(e)

$$I_m = \frac{100}{201} = 0.50 \text{ A}$$

(f)

$$I_m = \frac{100}{201.3} = 0.50 \text{ A}$$

(g) Both near or at resonance.

test  $\approx$  2R

(4)

(6.)

$$t = \frac{D}{C}$$

$$t = \frac{3.84 \times 10^8 \text{ m}}{3 \times 10^8 \text{ m/s}}$$


$$t = 1.28 \text{ (s)}$$

Name \_\_\_\_\_

Section \_\_\_\_\_

1. (40 POINTS) A single loop ( $N = 1$ ) of wire of radius  $r = 0.0300$  m lies with its face parallel to the page. It is in an external uniform perpendicular magnetic field pointing OUT as shown in the diagram below by the dot surrounded by a circle  $\odot$ . Suppose the external magnetic field magnitude is INCREASING with rate  $\Delta B/\Delta t = 10.00$  T/s.

- (a) (5 points) What is the area  $A$  of the wire loop?
- (b) (10 points) What is the magnitude  $|\varepsilon|$  of the voltage induced in the wire loop?
- (c) (10 points) The loop has resistance  $R = 40.0 \Omega$ . What is the current  $I$  in the loop?
- (d) (10 points) In the figure below, indicate the direction of the current  $I$ , clockwise or counter-clockwise, in the loop. Draw a labeled curved arrow on the loop representing the current direction.
- (e) (5 points) In the figure below, indicate the direction of the induced magnetic field, *in or out*. Indicate this direction by drawing a labeled IN  $\otimes$  or OUT  $\odot$  symbol within the circle.

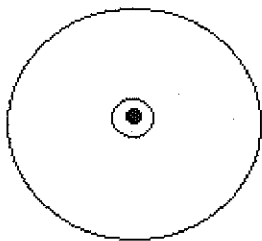

Name \_\_\_\_\_

Section \_\_\_\_\_

2. (40 points) The current  $I$  flowing rightward through inductor  $L$  is *increasing* at a steady rate of  $0.1280 \text{ A/s}$ . The magnitude  $|\mathcal{E}_L|$  of the voltage difference between the right end and the left end of the inductor is  $0.0160 \text{ (V)}$ .



(a) (30 points) What is the inductance  $L$ ?

(b) (10 points) Which end of the inductor above is at *higher* voltage, the left end or the right end? Explain.

Name \_\_\_\_\_

Section \_\_\_\_\_

3. (20 points) A transformer consists of 275 *primary* windings and 834 *secondary* windings. If the potential difference across the *primary* coil is 25.0 V,

- (a) (17 points) what is the voltage across the *secondary* coil?
- (b) (3 points) Is this a *step up* or *step down* transformer? Explain.
- (c) (5 points) EXTRA CREDIT. What is the effective load resistance of the secondary coil if it is connected across a  $125\ \Omega$  resistor?

Name \_\_\_\_\_

Section \_\_\_\_\_

**4. (30 POINTS) THE LC CIRCUIT.** A  $10.00\ \mu\text{F}$  capacitor  $C$  is initially charged to a voltage  $V$  of  $10.00\ \text{(V)}$ . It is then connected in series with an inductor  $L$ . Charge and current *oscillations* ensue.

- (a) (10 points) What is the *total* energy  $U$  of the circuit?
- (b) (10 points) If the *maximum* current in the inductor is  $I_m = 0.500\ \text{(A)}$ , then what is the inductance  $L$ ? What is the charge  $Q$  on the positive plate of the capacitor when the current reaches its maximum value  $I_m$ ?
- (c) (10 points) What is the angular frequency  $\omega$  of the charge oscillations?



Name \_\_\_\_\_

Section \_\_\_\_\_

**5. (40 points). Compute the impedance  $Z$  of a series R-L-C circuit at angular frequencies  $\omega =$**

**(a) (6 points) 1001 rad/s**

**(b) (6 points) 751 rad/s**

**(c) (6 points) 502 rad/s.**

**Assume  $R = 201 \, \Omega$ ,  $L = 0.902 \, \text{H}$  and  $C = 2.01 \, \mu\text{F}$ .**

**(d) (6 points) What is the resonant angular frequency  $\omega_{\text{RES}}$  of the circuit?**

**Assume the voltage source amplitude is  $V_m = 100.00 \, (\text{V})$ .**

**(e) (6 points) What is the current amplitude  $I_m$  when the circuit is at the resonant angular frequency?**

**(f) (5 points) What is the current amplitude  $I_m$  when the circuit is at 751 rad/s?**

**(g) (5 points) Should the answers to (e) and (f) be nearly equal? Explain.**

Name \_\_\_\_\_

Section \_\_\_\_\_

**6. EXTRA CREDIT. (10 POINTS)** How much time  $t$  (in seconds) does it take light to travel from the Moon to the Earth, a distance  $D = 384,000$  km? Assume the speed of light is  $c = 3.00 \times 10^8$  m/s.