

Physics
ZB


CH 22

3-25-13

AC circuits

Alternating current

R and source only

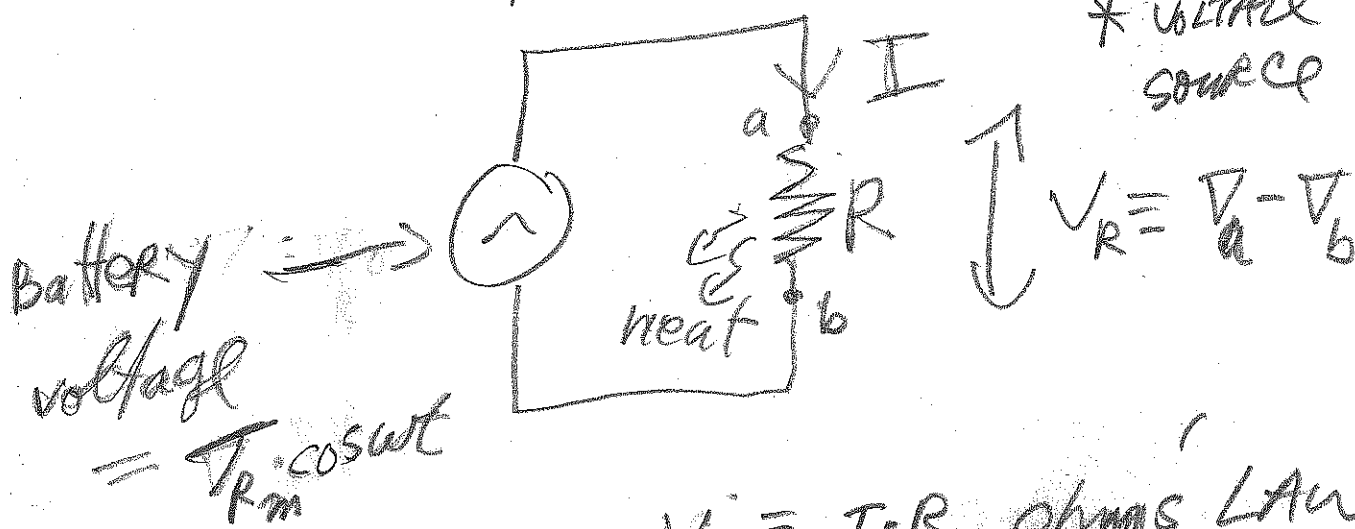


$V_R = I \cdot R$ Ohm's Law

$$I = \frac{V_R}{R} = \frac{V_{Rm} \cos \omega t}{R}$$


$$I = \frac{V_{Rm} \cos \omega t}{R}$$

$$I = I_m \cos \omega t$$

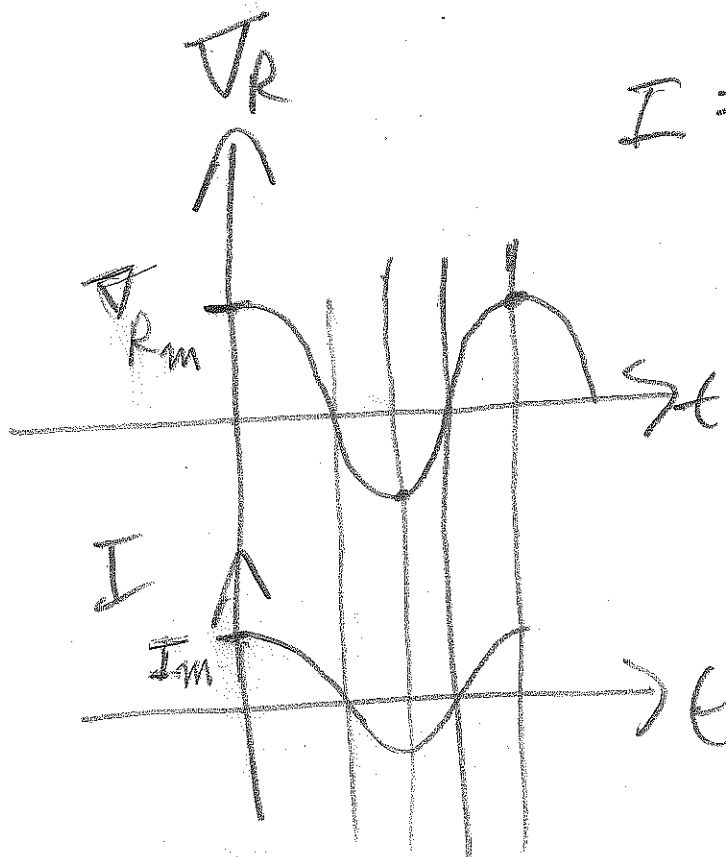


I and V_R are in phase

PHASORS = vectors

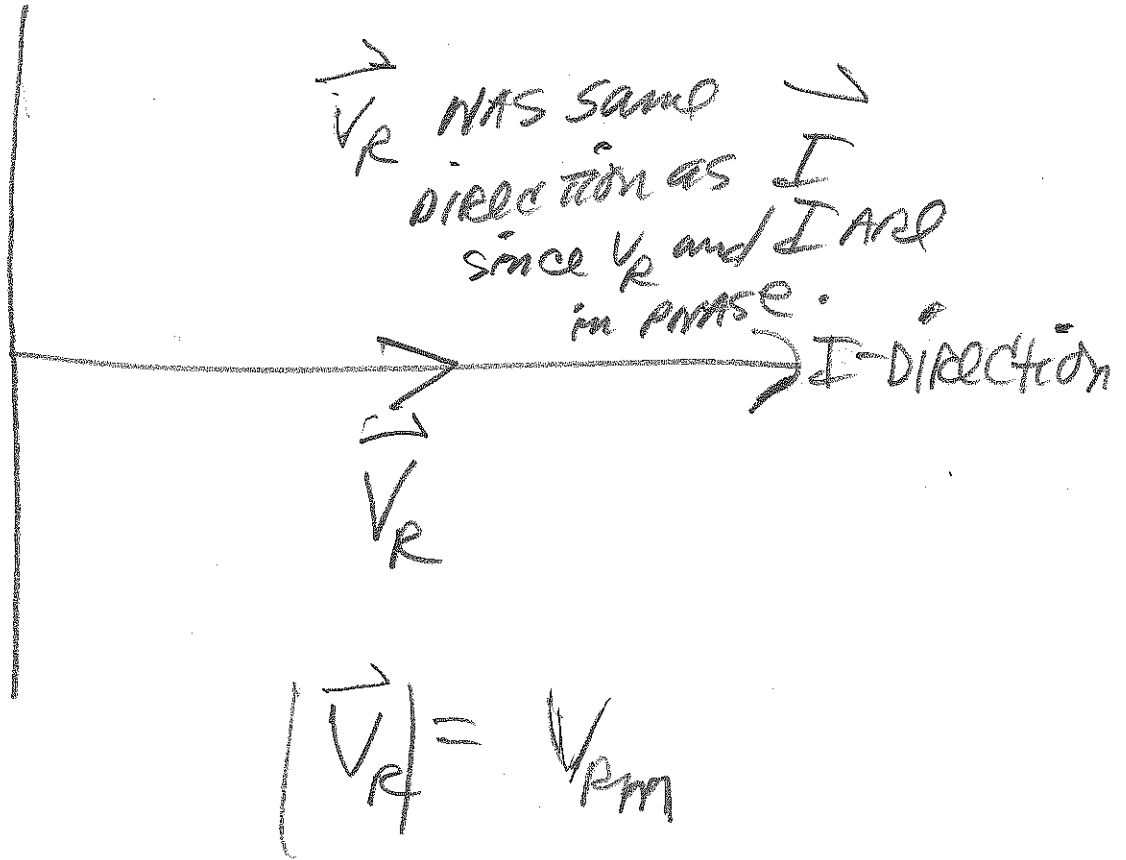

Inductor and SOURCE ONLY*

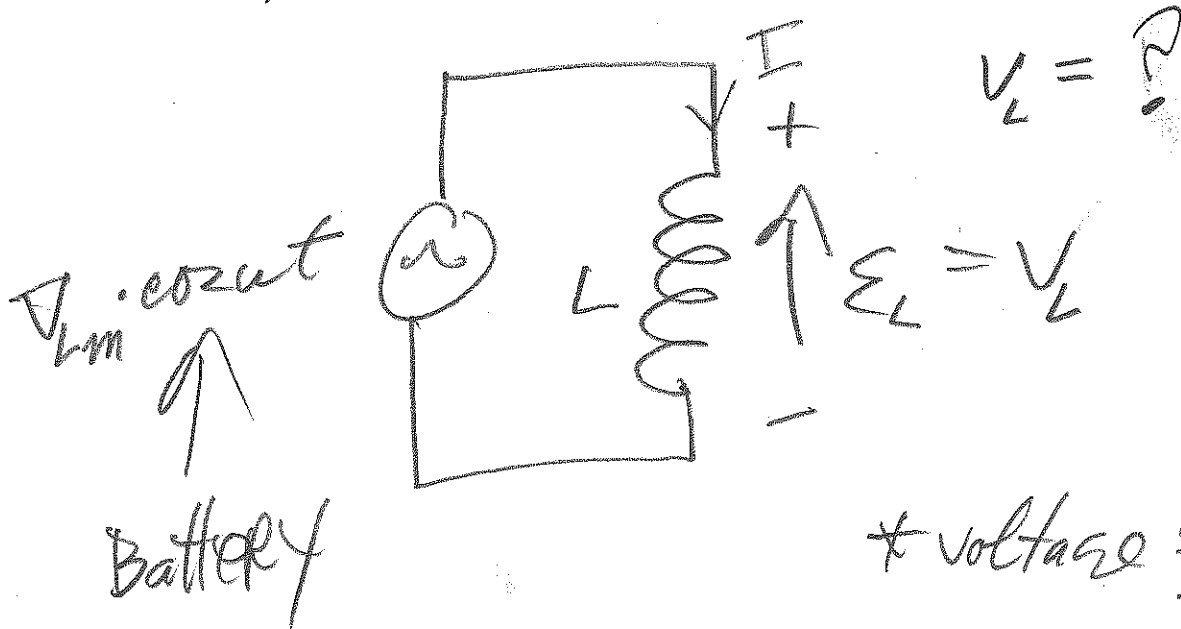

Background to Inductor and source:

$$\underline{Z_A}$$

$$F_x = ma_x$$


$$\underline{Z_B}$$

$$V_L = L \cdot \frac{\Delta I}{\Delta t}$$

$$F_x = m \frac{\Delta v}{\Delta t}$$




Since mass "has inertia",
the velocity
does not
change immediately
with applied force:
inertial time lag.

Example: $F_x = 2(N)$

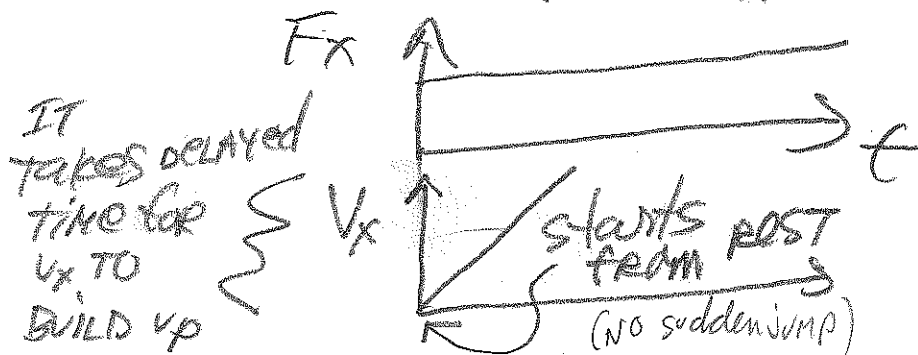



$$2(N) = m \frac{\Delta v_x}{\Delta t}$$

$$v_x = \frac{2(N)}{m} \cdot t$$

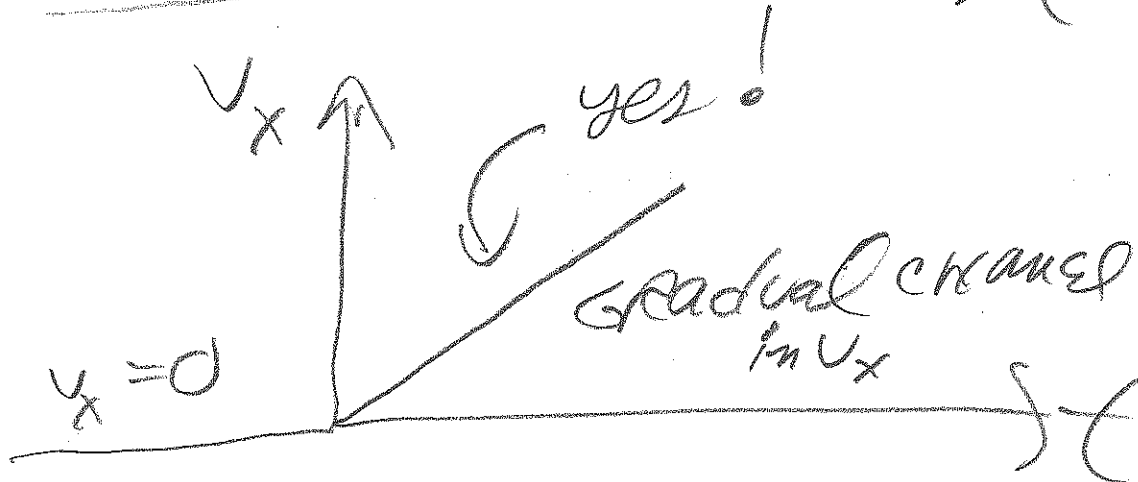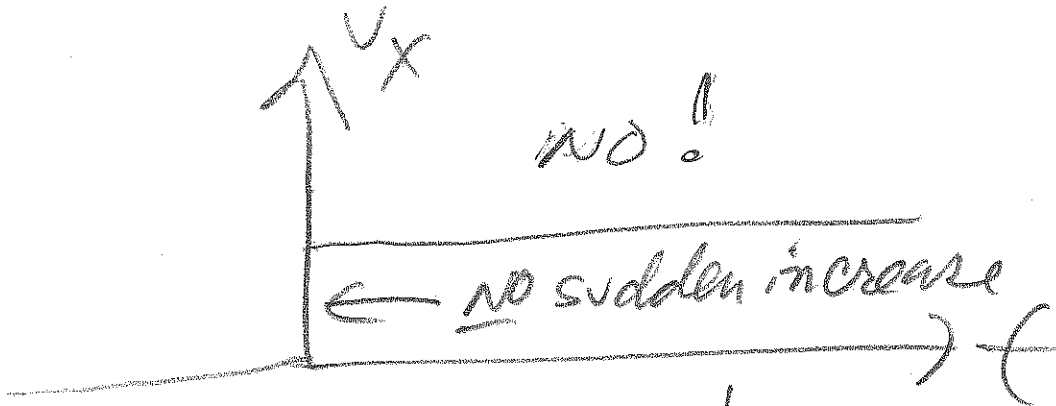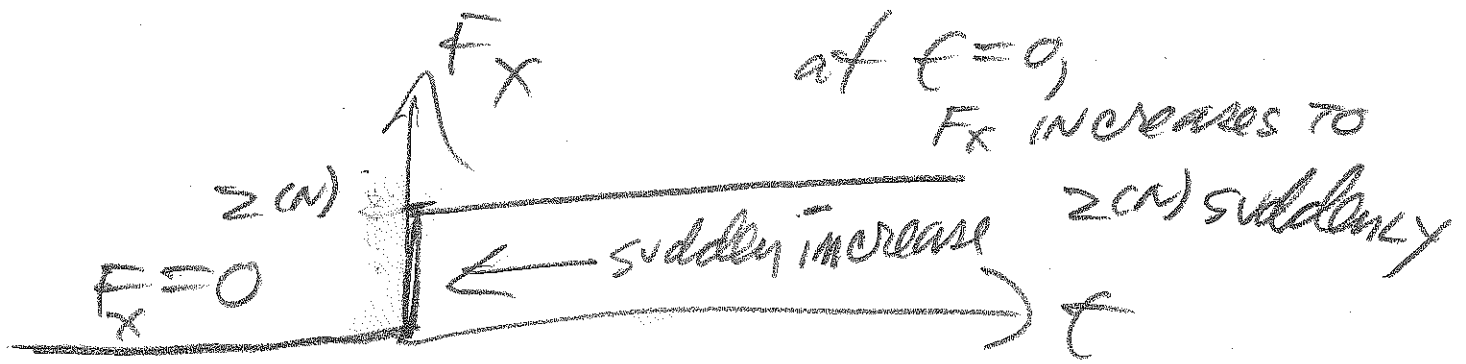

GO BACK TO L circuit:

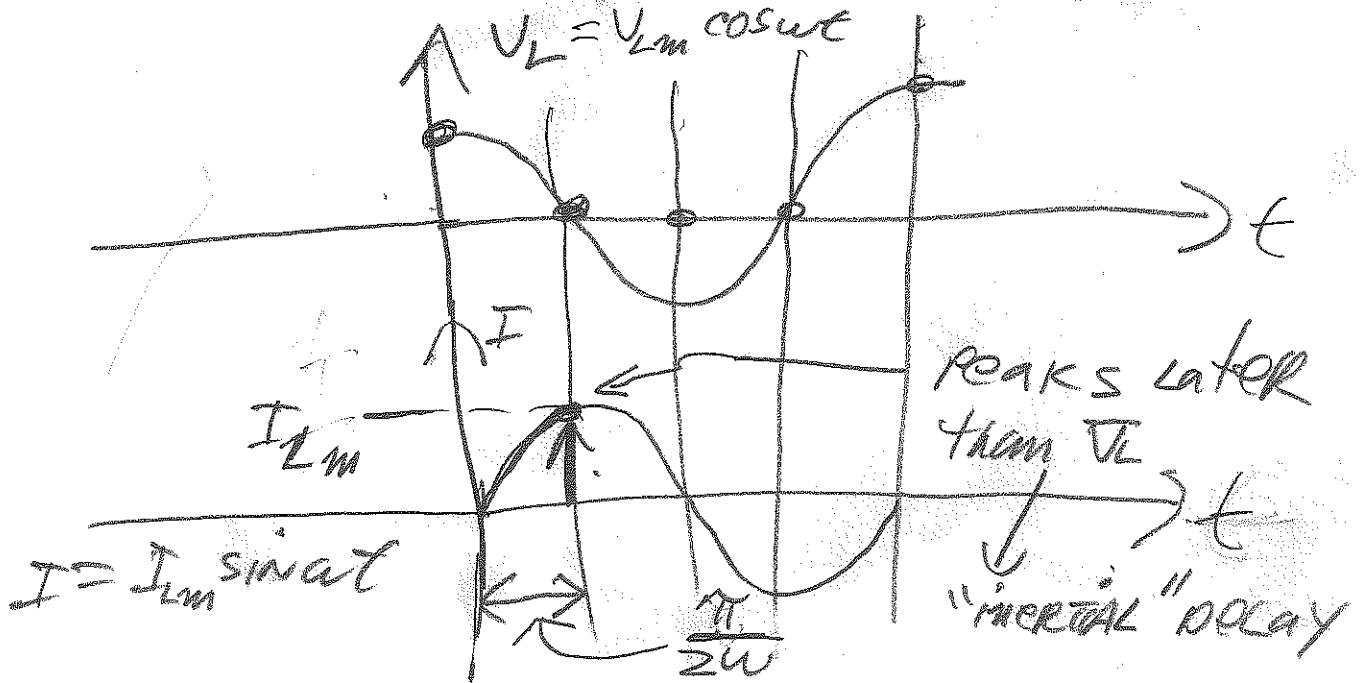

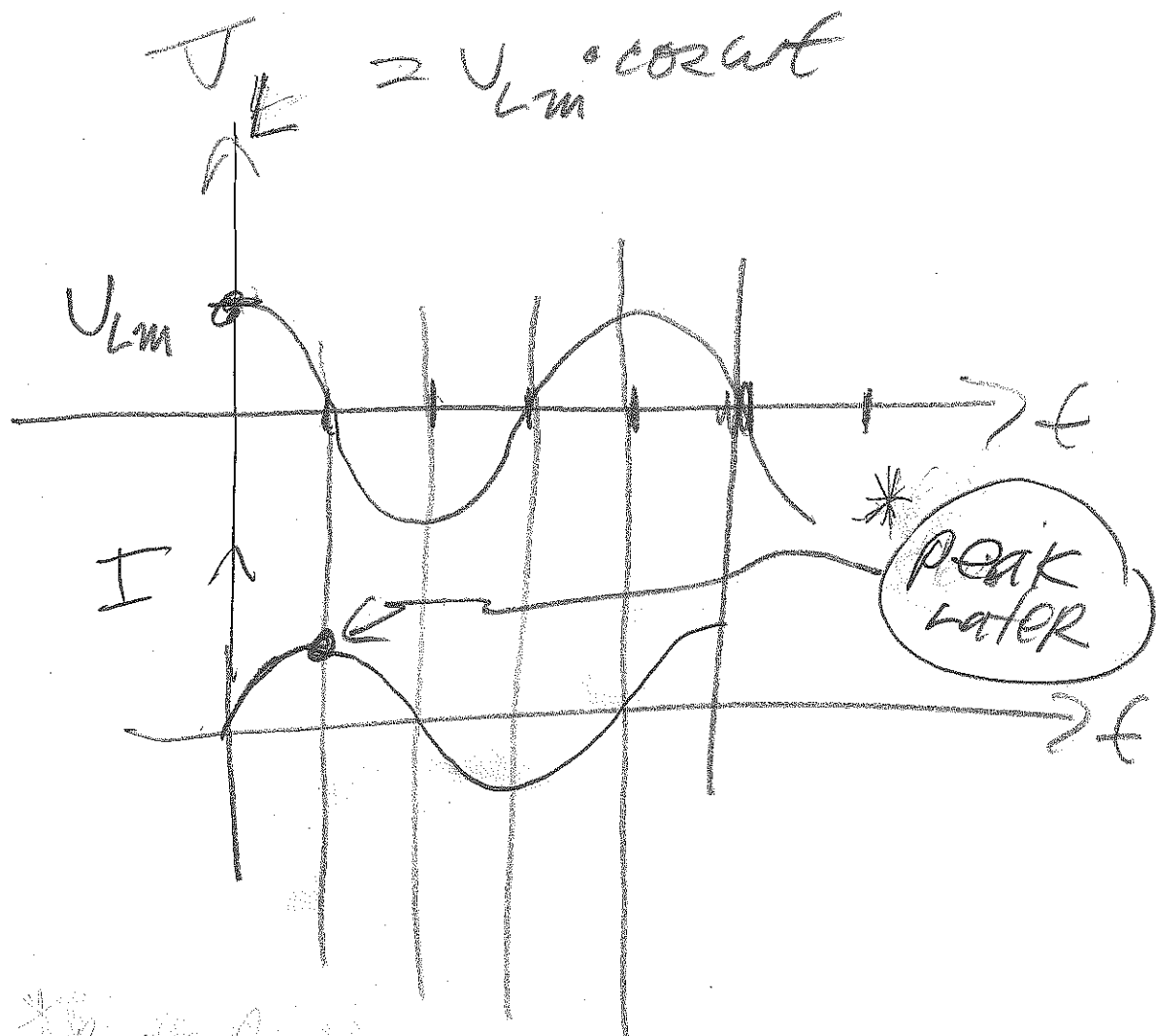

* Peak later

Because of the "inertia" of L ,
the current I lags V_L .

Table of correspondence

ZA	ZB
mass (m)	L (inductance)
position x	q (charge)
velocity v_x	i (current)
force F	voltage
spring constant k	$\frac{1}{C} = \frac{1}{\text{capacitance}}$

$$I_{Lm} = \frac{V_{Lm}}{X_L}$$



$$X_L = \omega \cdot L$$

note: when ω is large
 I_{Lm} is small.

↑
 reactance


$$I = \frac{V_{Lm}}{X_L} \sin \omega t = I_m \sin \omega t$$

Phasor diagram:

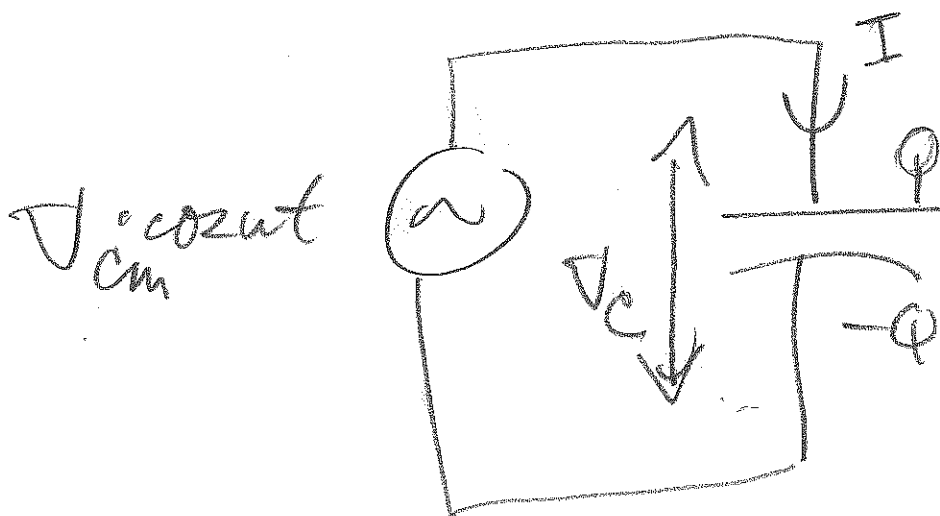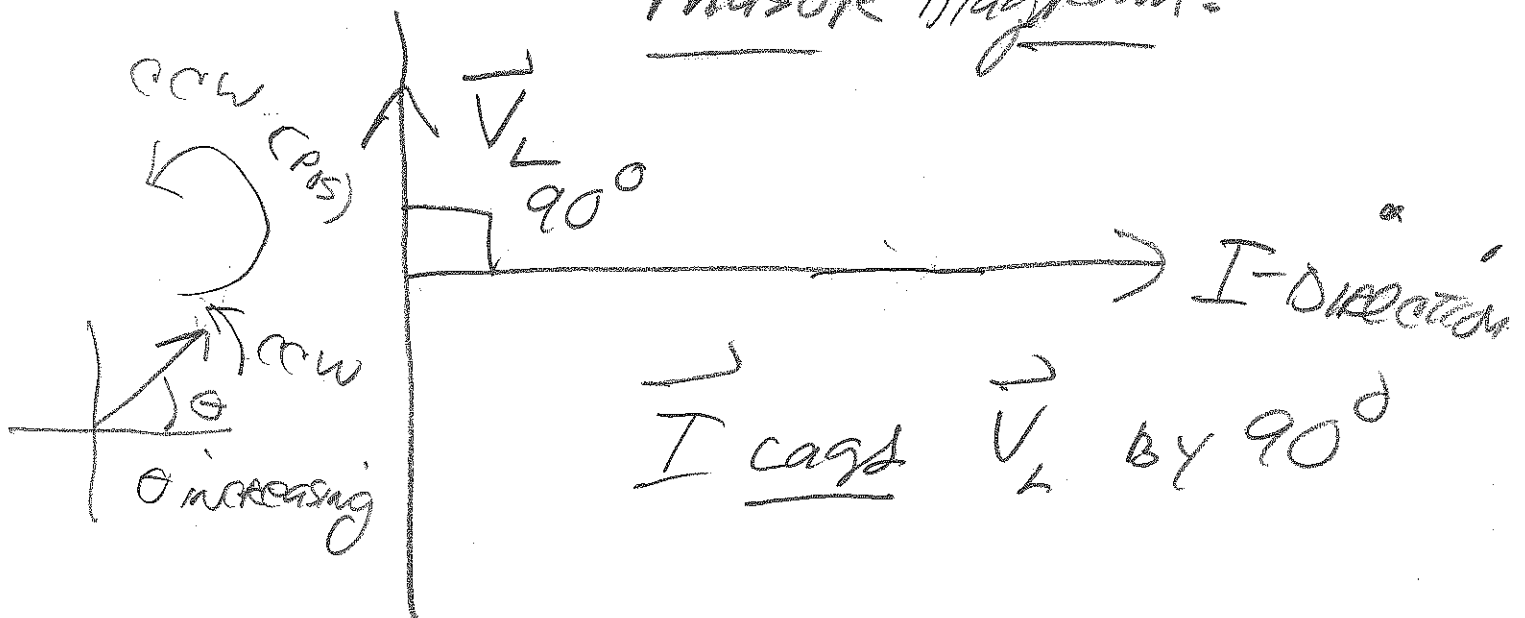

C and source only:

I leads V_C by 90°

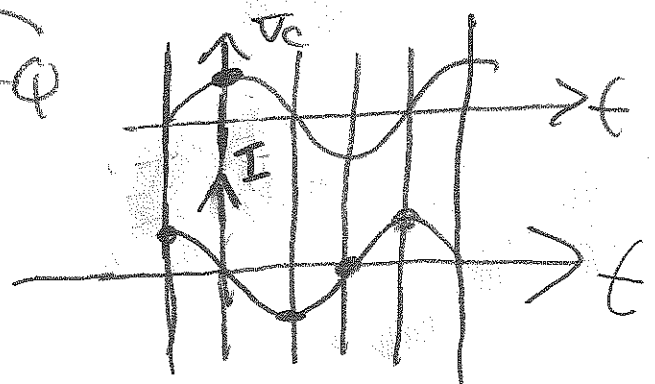

$$I = \frac{\Delta Q}{\Delta t} = C \frac{\Delta V_C}{\Delta t}, \Delta V_C = \text{change in VOLTAGE}$$


$$I = I_{cm} \sin \omega t = -\omega C V_{cm} \cos \omega t$$

I Leads V_C by 90°

$$I_{cm} = \frac{V_{cm}}{X_C}, \quad X_C = \frac{1}{\omega C}$$

Note: as C gets large, I_{cm} get large.

↑
Reactance

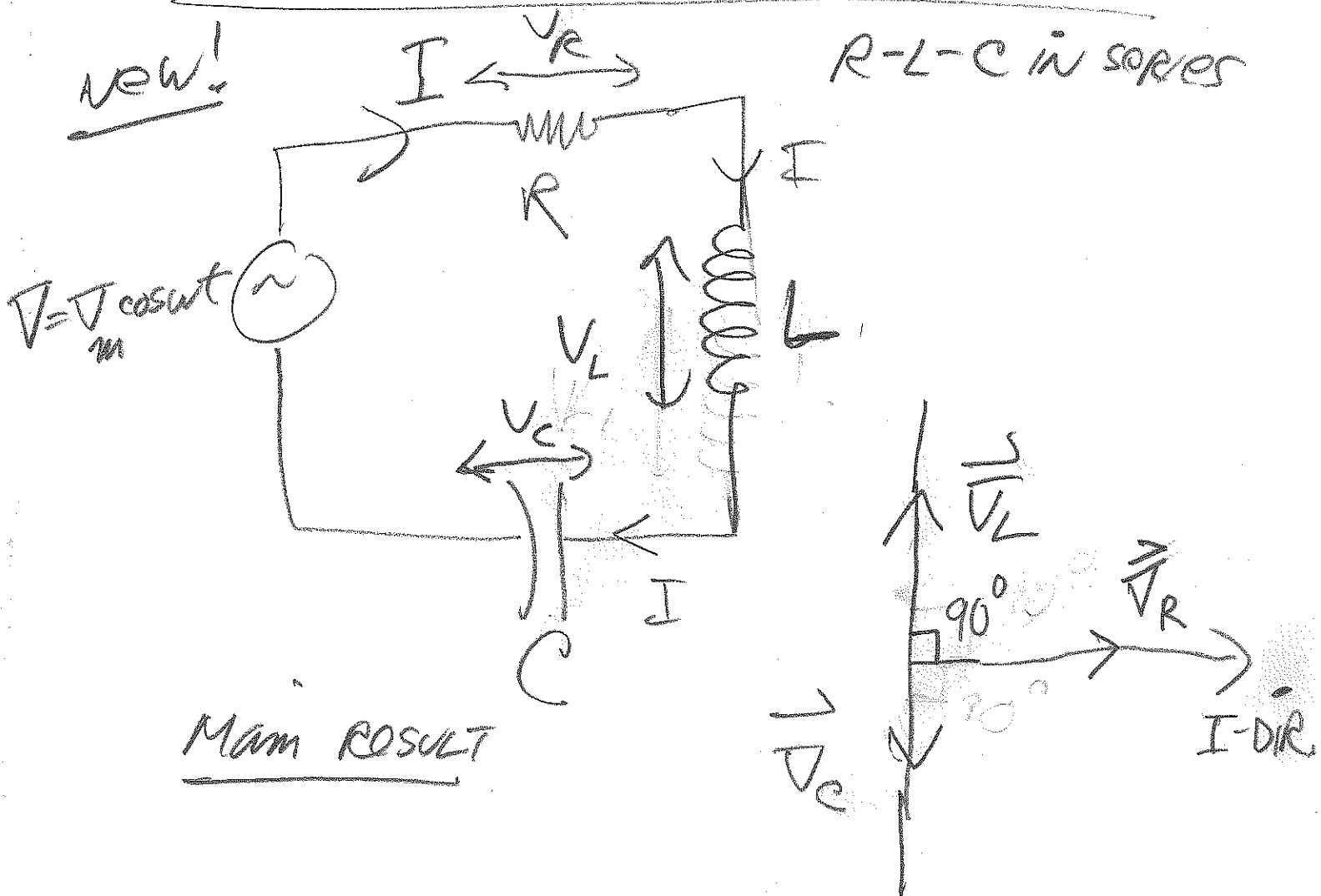

$$I = I_m \cos(\omega t - \phi)$$

$$I_m = \frac{V_m}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}$$

↑
complicated
Phase function

$$= \frac{V_m}{Z}, \quad Z = \text{impedance}$$

$I_m = \text{maximum at resonance:}$

$$\omega L - \frac{1}{\omega C} = 0$$

$$\omega = \frac{1}{\sqrt{LC}} = \text{natural frequency}$$

$$I_{m_{\text{MAX}}} = \frac{V_m}{R}$$

*) see Thevenin Fall's
bridge collapse on
V-TUBE: velocity, like
current I

as R get small, $I_{m_{\text{MAX}}}$ is large.