

3-5-14

Preface to CAPACITORS in CH24 CH23 REVIEW

$$\vec{E} = -\frac{\partial V}{\partial x} \hat{i} - \frac{\partial V}{\partial y} \hat{j} - \frac{\partial V}{\partial z} \hat{k}$$

$$= \left(-\frac{\partial V}{\partial x}, -\frac{\partial V}{\partial y}, -\frac{\partial V}{\partial z} \right)$$

$$\vec{E} \cdot d\vec{l} = E_x dx + E_y dy + E_z dz$$

$$d\vec{l} = (dx, dy, dz)$$

$$= dx \hat{i} + dy \hat{j} + dz \hat{k}$$

$$\Delta V = V_B - V_A = - \int_A^B \vec{E} \cdot d\vec{l} \quad *$$

$$* \quad \vec{W} = -\Delta U$$

$$\vec{W} = q \int_A^B \vec{E} \cdot d\vec{l} \quad \text{If } \Delta U = -\vec{W} :$$

$$\Delta U = -q \int_A^B \vec{E} \cdot d\vec{l} \Rightarrow \Delta V = \frac{\Delta U}{q} = - \int_A^B \vec{E} \cdot d\vec{l}$$

WORK by
FIELD


3-5-14

CAPACITORS ch 24

any 2 oppositely charged

conductors.

CAPACITOR

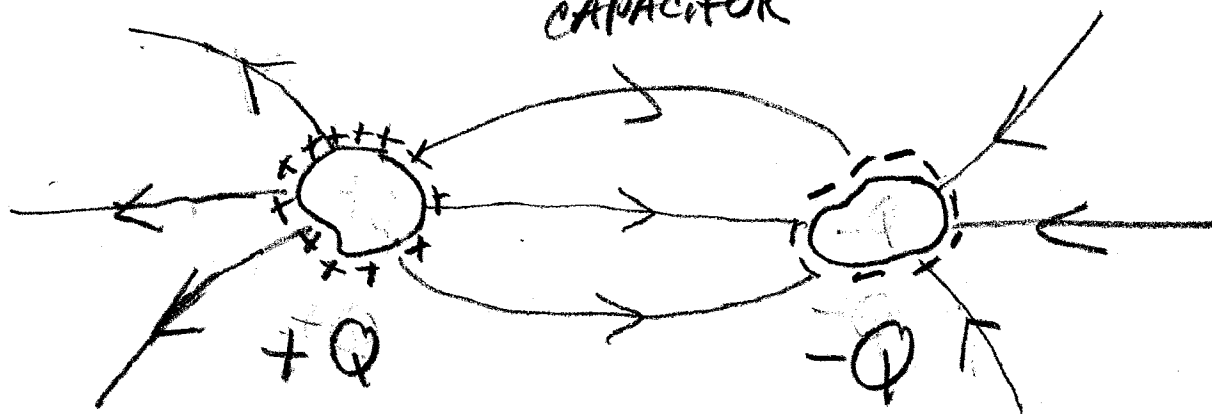

note: $|+Q| = |-Q| = |Q|$ = SAME magnitude


$$\text{CAPACITANCE} = C \equiv \frac{Q}{\Delta V} = \frac{Q}{V_+ - V_-}$$

V_+ = potential of positive conductor
 V_- = potential of negative conductor.

NOTE:


a conductor is an
EQUIPOTENTIAL object.

$V = \text{constant}$ on
conductor.

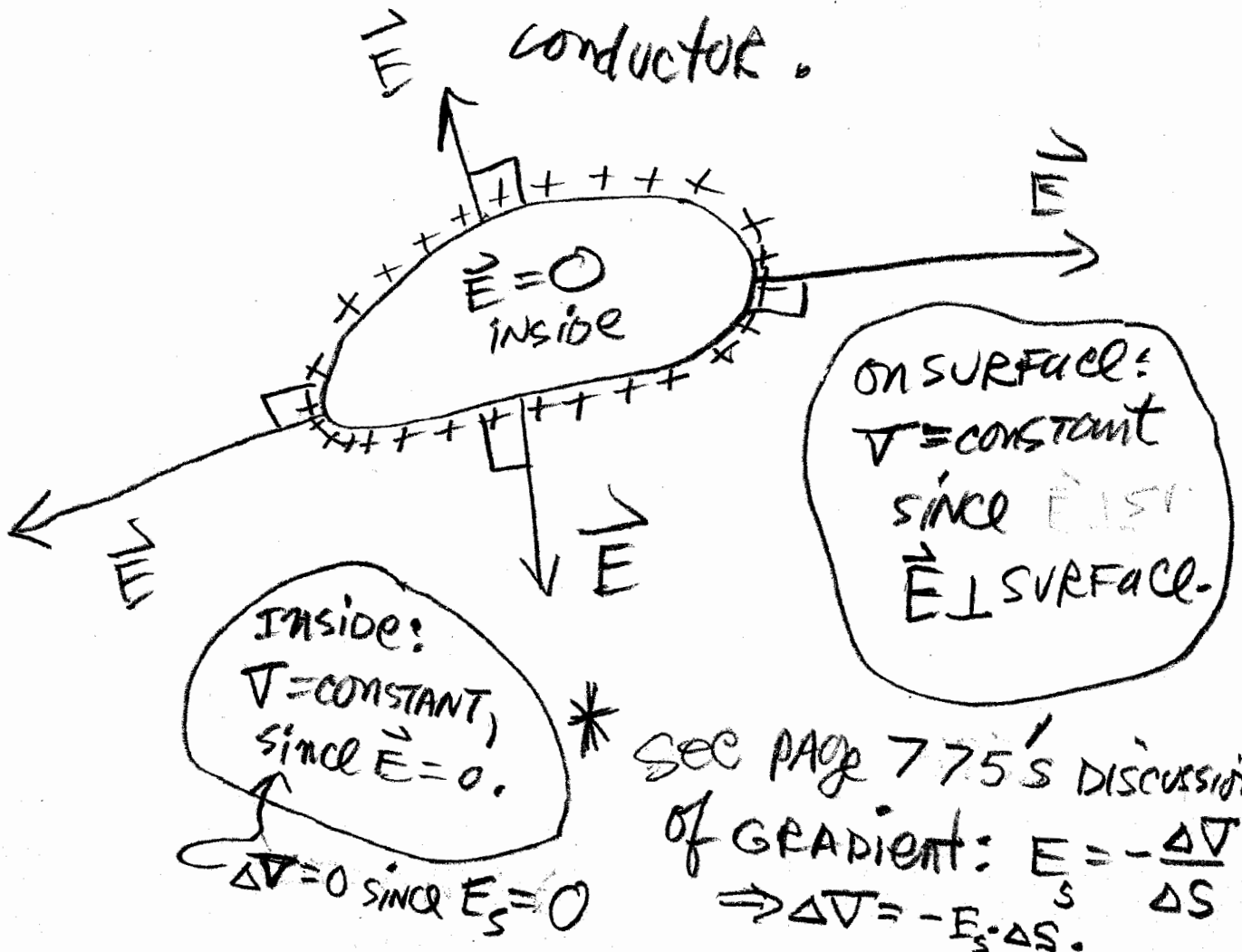

$$C = \frac{Q}{E \cdot d}, \text{ where } E = \frac{Q}{A \epsilon_0}$$
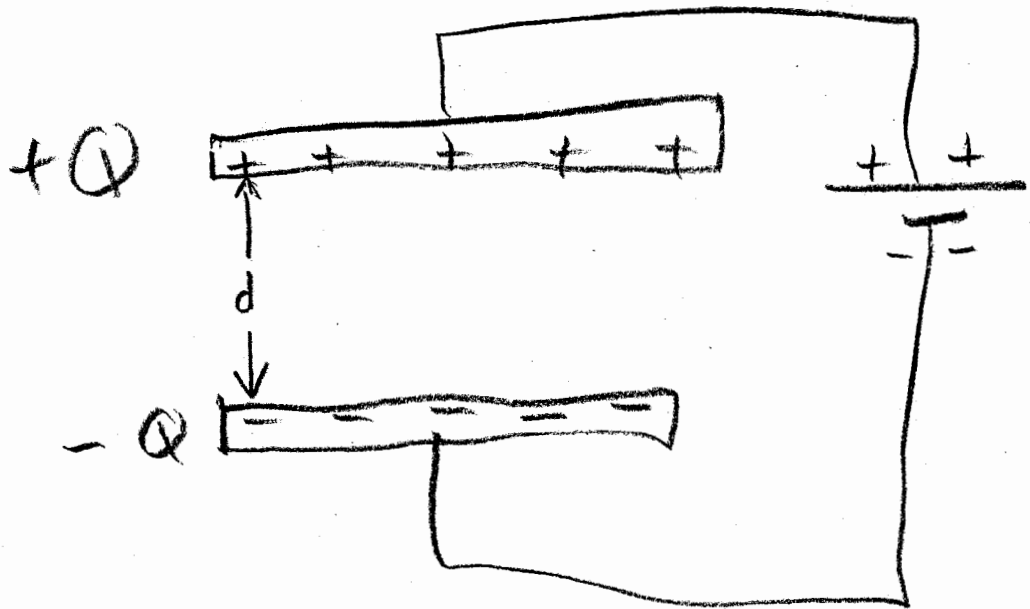
$$\Rightarrow C = \frac{Q}{\left(\frac{Q}{A \epsilon_0}\right) \cdot d} = \boxed{\frac{A \epsilon_0}{d}}$$




note: C is independent of Q .
It's only a function geometry.

3-5-14

1

Capacitors

example

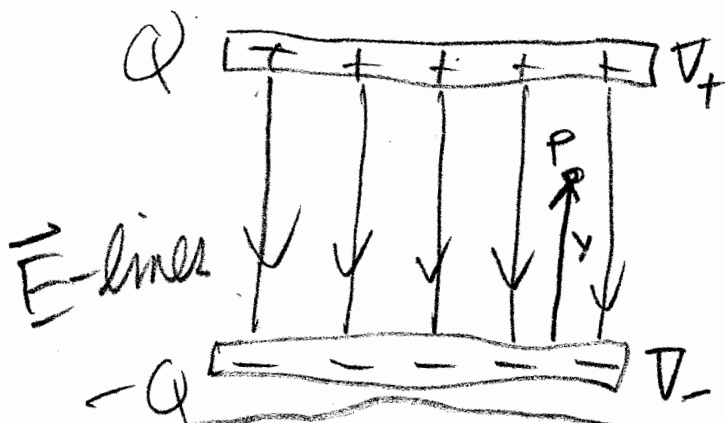

(a) FIND C.

$$C = \frac{A\epsilon_0}{d}$$

$$= \frac{(2\text{m}^2)(8.85 \times 10^{-12} \frac{\text{F}}{\text{m}})}{5 \times 10^{-3} \text{cm}}$$

$$= 3.54 \text{ nF}$$

$$C = \frac{Q}{V_+ - V_-} \text{ (F)}$$

FARAD

$$V \text{ at } P = E \cdot y$$

$$V_- \equiv 0$$

$$V_+ = E \cdot d$$

$$(y = d)$$



12

(b) FIND CHARGE ON EACH PLATE.

TOP PLATE: Q

bottom " : $-Q$

$$\Delta V = V_+ - V_- = 10.0 \times 10^3 \text{ (V)}$$

$$\text{kV} = 10^3 \text{ (V)}$$

$$Q = C \cdot \Delta V = 3.54 \times 10^{-9} \text{ F} \cdot (10.0 \times 10^3 \text{ V})$$

$$= \underbrace{(3.54 \times 10^{-5} \text{ (F)})}_{\text{circled}} 10^4$$

$$= 35.4 \times 10^{-6} \text{ (F)}$$

$$= 35.4 \text{ nF}$$

(c) $E = |\vec{E}| \Rightarrow$


$$\Delta V = V_+ - V_- = E \cdot d - E \cdot 0$$

$$10.0 \times 10^3 \text{ V} = E \cdot d$$


$$E = \frac{10.0 \times 10^3 \text{ (V)}}{5 \times 10^{-3} \text{ (m)}} \\ = 2 \times 10^6 \left(\frac{\text{V}}{\text{m}} \right)$$

Sec. 24.2
SERIES

C_1 C_2

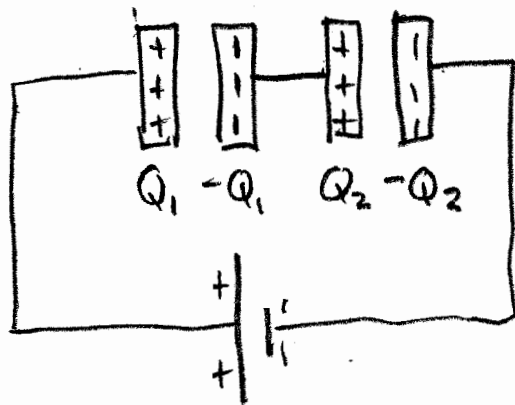

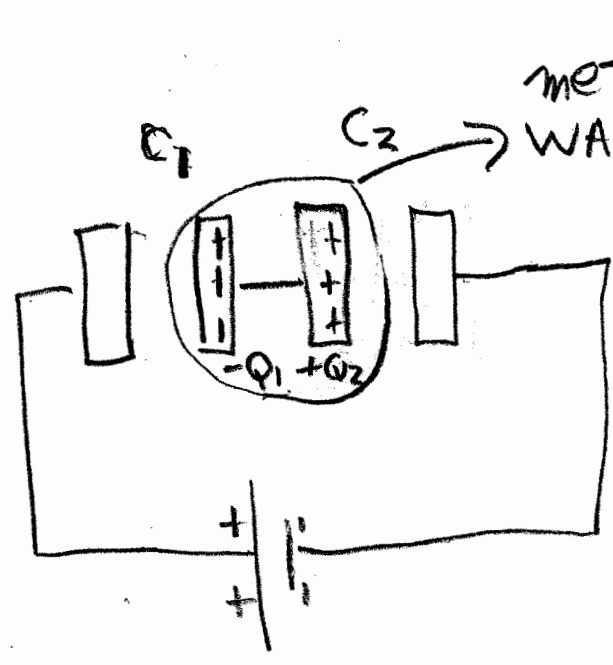\longleftrightarrow
 $\Delta V = V_+ - V_-$





BEFORE BATTERY:

THUS;

$$|-Q_1| = |Q_2|$$

$$|-Q_1| = |Q_2| = Q$$

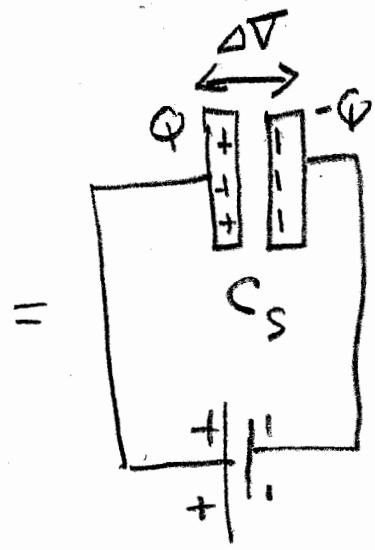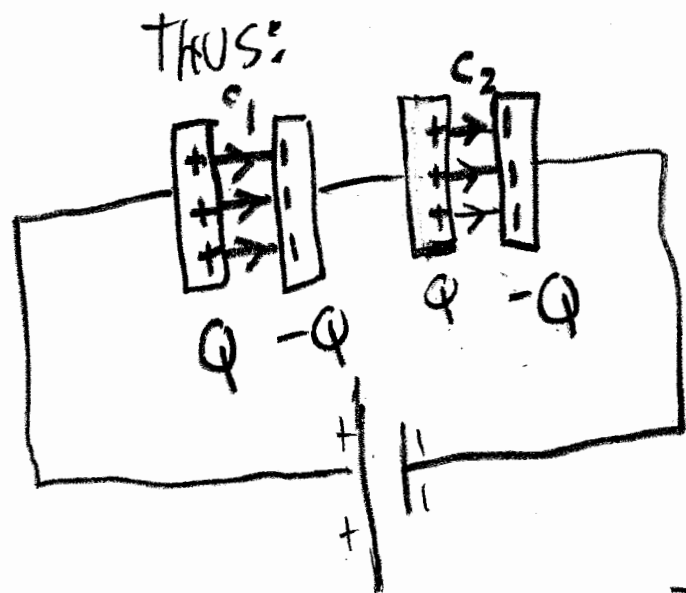

$$\left. \begin{array}{l} \Delta V_1 = \text{VOLTAGE ACROSS } C_1 \\ \Delta V_2 = \text{ " " } C_2 \end{array} \right\} \begin{array}{l} \Delta V = \Delta V_1 + \Delta V_2 \\ \frac{Q}{C_s} = \frac{Q_1}{C_1} + \frac{Q_2}{C_2} \end{array}$$

C5

$$Q_1 = Q_2 = Q$$

$$\frac{Q}{C_S} = \frac{Q}{C_1} + \frac{Q}{C_2}$$


$$\frac{1}{C_S} = \frac{1}{C_1} + \frac{1}{C_2}$$

Series :

$$\rightarrow C_S = \frac{C_1 \cdot C_2}{C_1 + C_2} < C_2$$

$$C_S = \frac{C_1 \cdot C_2}{C_1 + C_2} < C_1$$

parallel

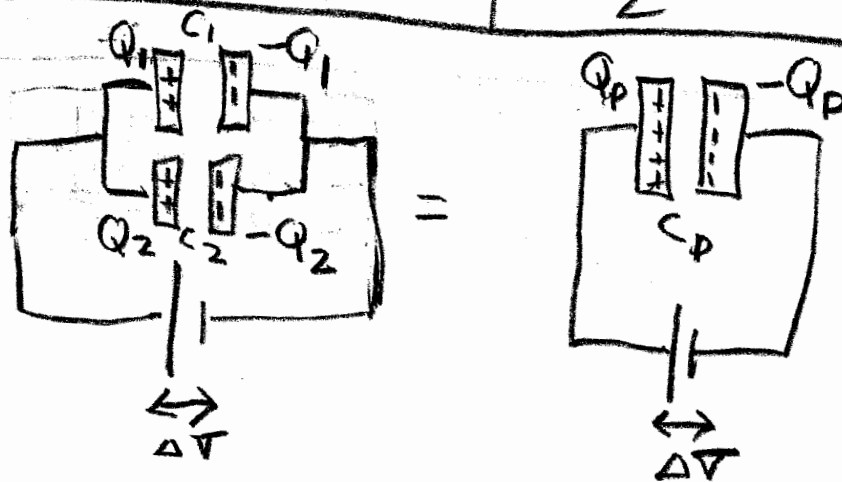

(6)

$$\Delta V_1 = \Delta V_2 \text{ and } Q_p = Q_1 + Q_2$$

$$Q_p = Q_1 + Q_2$$


$$C_p \cdot \Delta V = C_1 \cdot \Delta V_1 + C_2 \cdot \Delta V_2$$

$$\Delta V_1 = \Delta V_2 = \Delta V$$

~~$$C_p \cdot \Delta V = C_1 \cdot \Delta V + C_2 \cdot \Delta V$$~~

$$C_p = C_1 + C_2$$


EXAMPLE

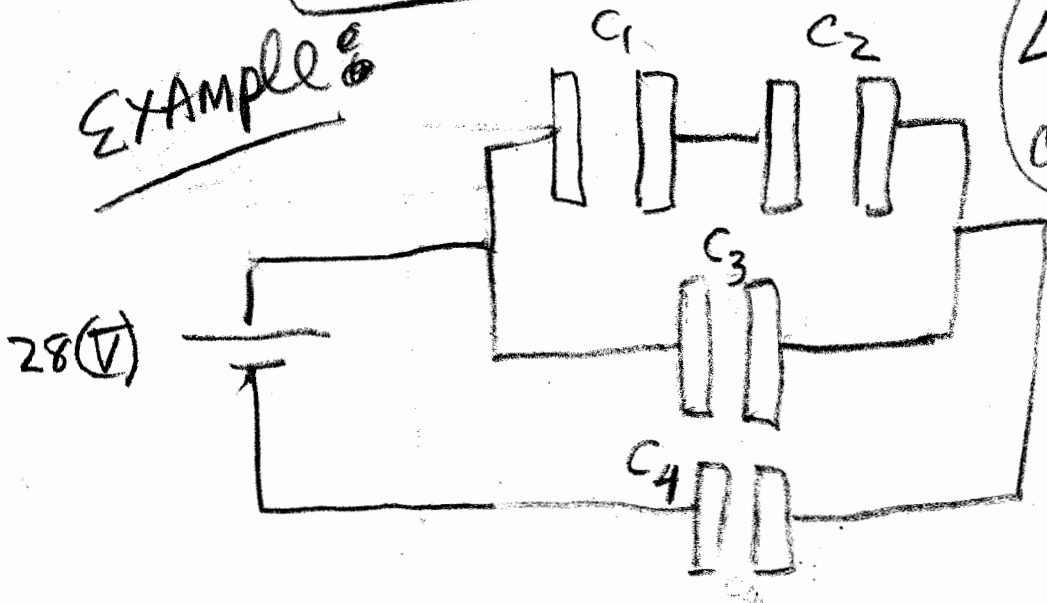

4 identical CAPACITORS

7


$$C_1 = C_2 = C_3 = C_4 = 4 \mu F$$

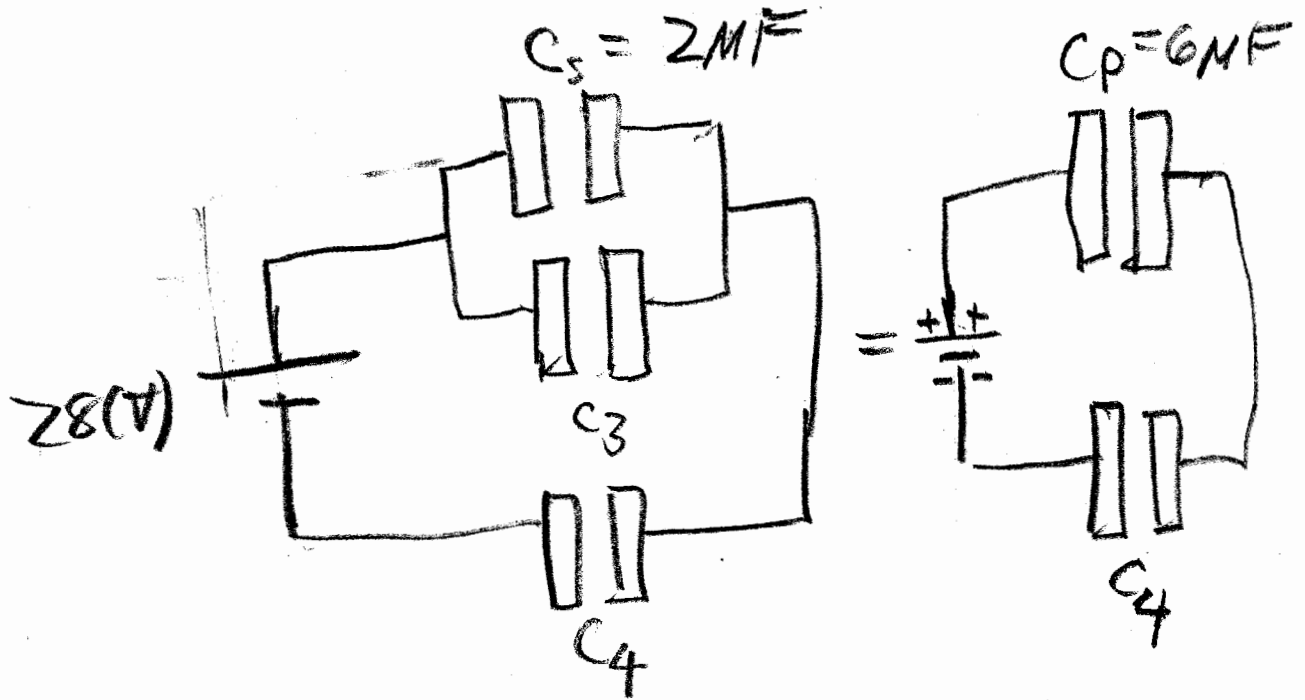

$$C_s = \frac{C_1 \cdot C_2}{C_1 + C_2} = \frac{(4 \cdot 4)}{4 + 4} = \frac{16}{8} = 2 \mu F$$

$$C_p = C_s + C_3 = (2 + 4) \mu F = 6 \mu F$$

8

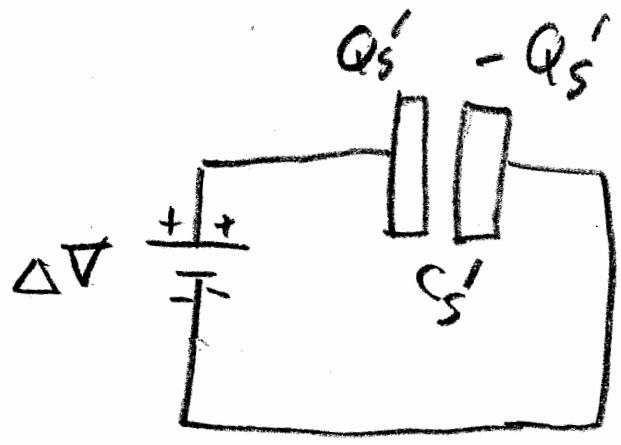

$$C'_S = \frac{C_p \cdot C_4}{C_p + C_4}$$

$$C'_S = \frac{(0) \cdot (4)}{0 + 4} = \frac{24}{10} \mu F$$


$$C'_S = 2.4 \mu F$$

$$\Rightarrow Q'_S = C'_S \cdot \Delta V$$


$$= (2.4 \times 10^{-6}) (28) (C)$$

$$= 67.5 \mu C$$

Note: $\mu C = 10^{-6} C$

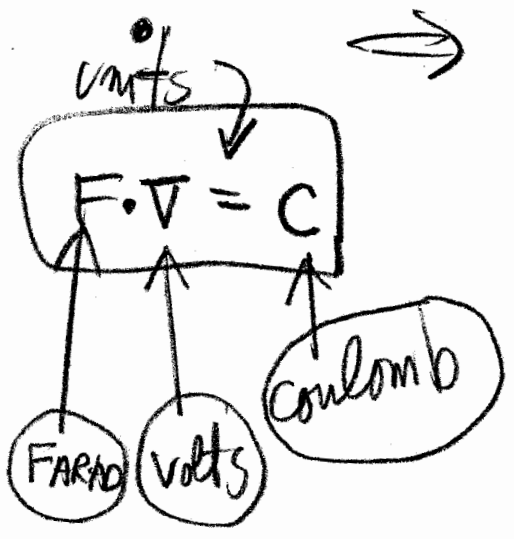

3-5-14

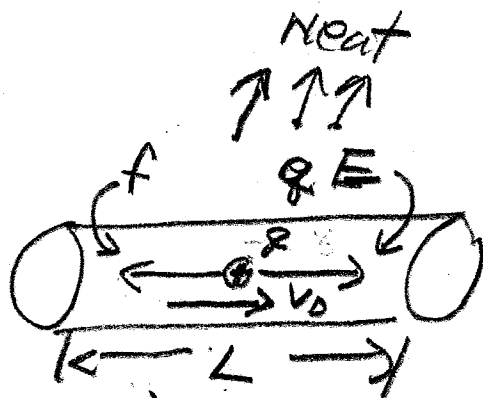

$v_D = \text{DRIFT speed}$


$f = \text{"friction" force.}$

$W_f = -f \cdot L = \text{friction work}$

$P2A/4A$

$\text{heat} = f \cdot L = -W_f$


$P2A/4A$: Example: Heat

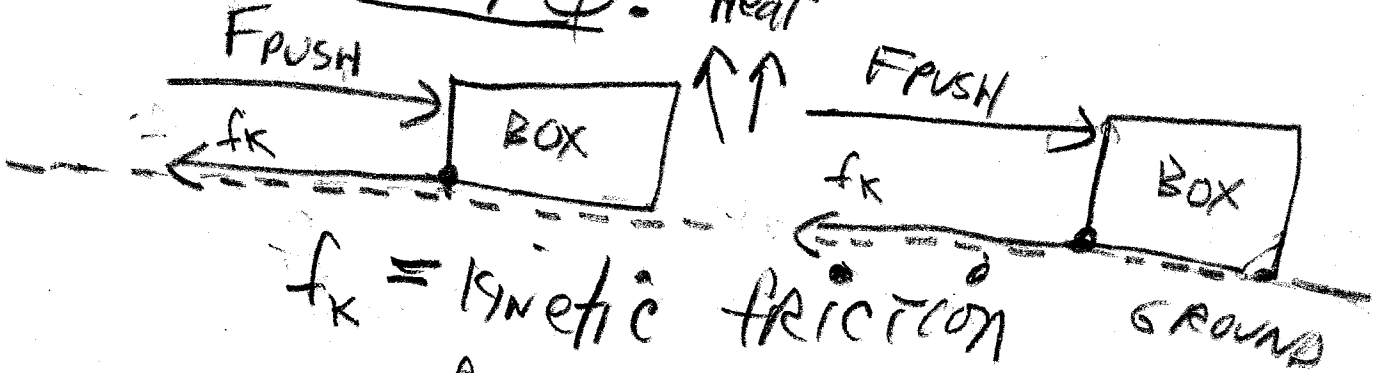

$f_k = \text{kinetic friction force.}$

$\text{HEAT} = f_k \cdot \text{DISTANCE}$


RC circuits

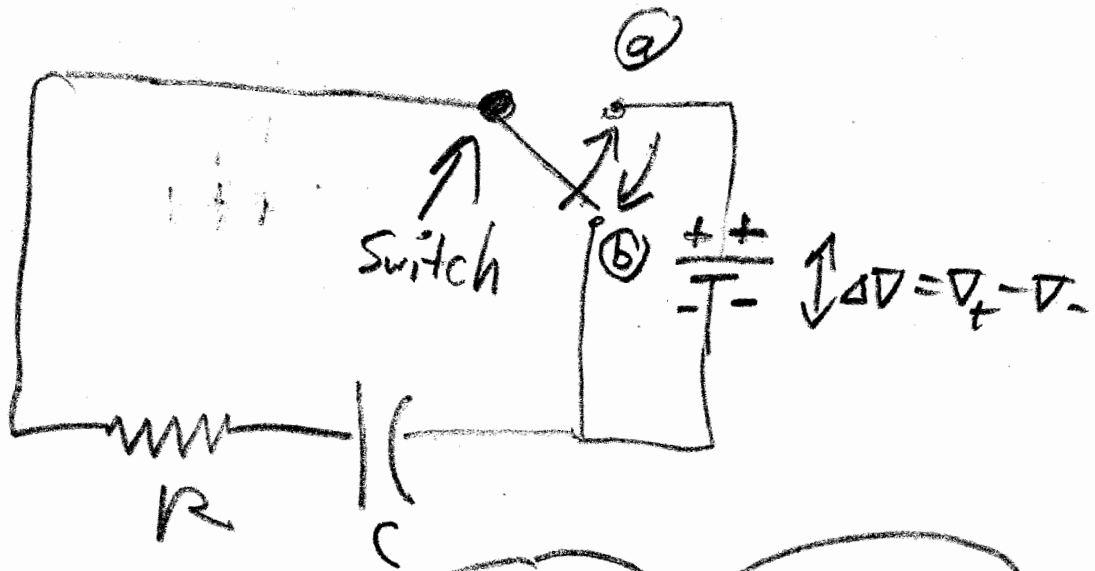

switch at (a) :

I FLOWS; heat is generated and Q increases.

ASSUME $Q=0$ at $t=0$

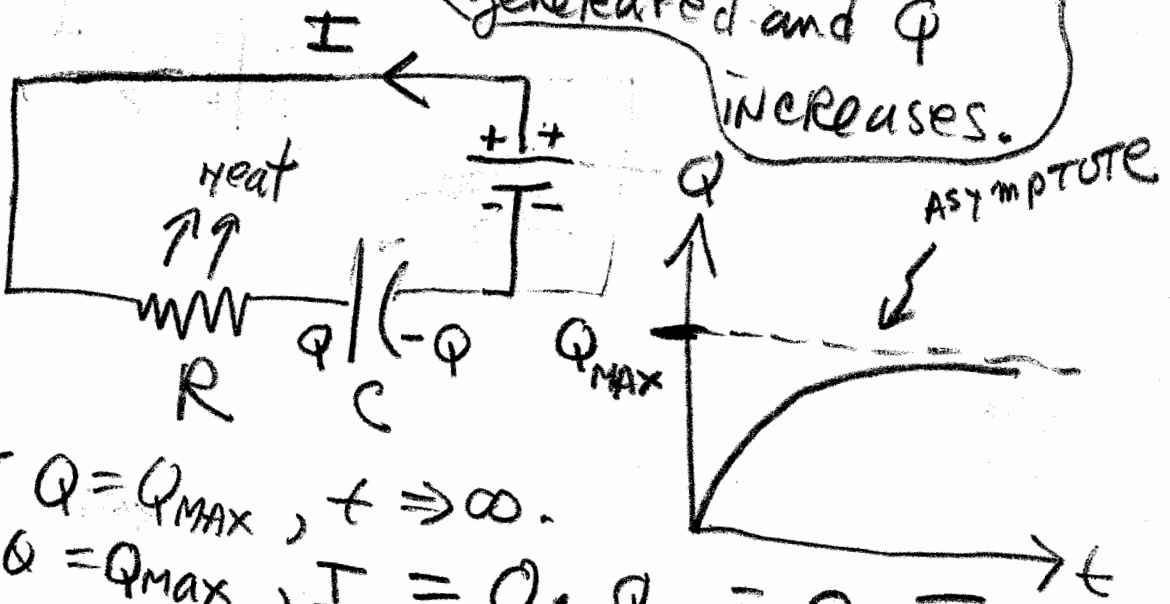

AT $Q = Q_{MAX}$, $t \Rightarrow \infty$.

AT $Q = Q_{MAX}$, $I = 0$; $Q_{MAX} = C \cdot \Delta V$

CHARGING circuit:

$$Q = Q_{MAX} \left(1 - e^{-t/RC} \right)$$

at $t=0$: $e^{-0} = 1 = e^0$


$$Q = Q_{MAX} \cdot (1-1) = 0$$

at $t=\infty$: $e^{-\infty} = 0$

$$Q = Q_{MAX} \cdot (1-0) = Q_{MAX}$$

DIS-CHARGING: switch at (b)

Q decreases

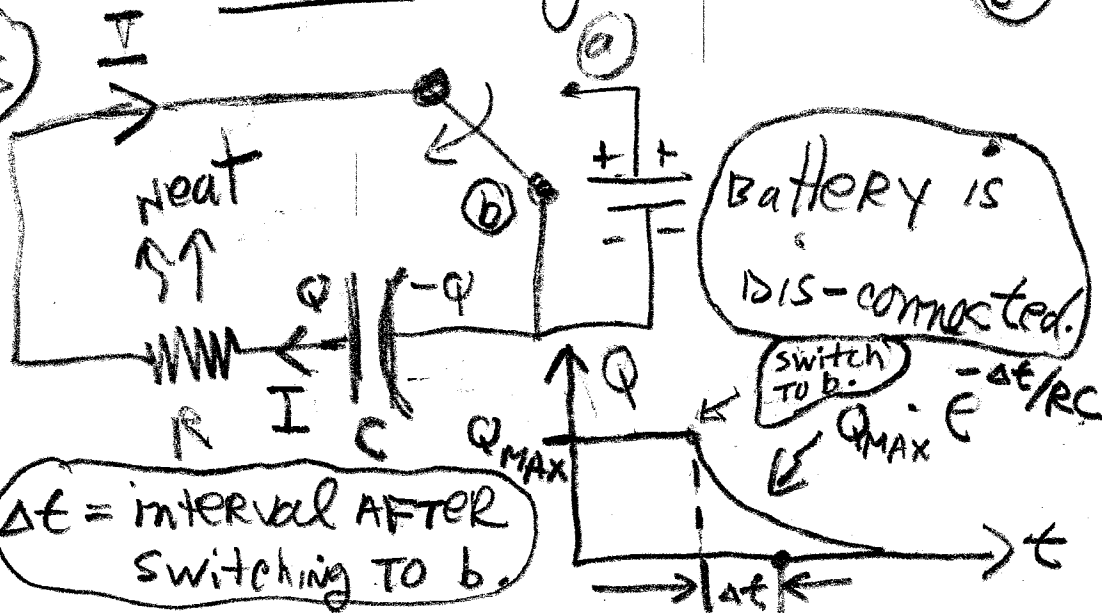

GLOBAL EXAM schedule

ZB March 21 = Test 2

Review: MAR 17

CH 18, 19, 20



end only

Assigned

4B March 21

CH 23, 24