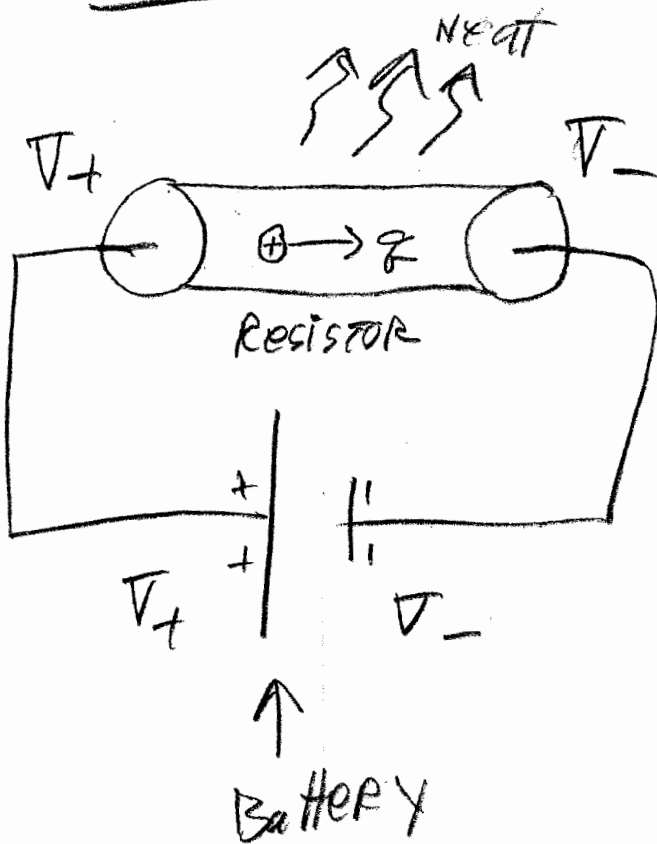


Power: sec. 25.5 3-10-14 (1)



Inside RESISTOR:  $q$  LOSES  
POTENTIAL ENERGY TO HEAT:

$$q \cdot (V_+ - V_-) = |\Delta U_{\text{LOST}}|$$

Inside BATTERY (see FIG 25.13):

$q$  GAINS POTENTIAL ENERGY DUE TO  
CHEMICAL REACTION:  $q \cdot (V_- - V_+) = \Delta U_{\text{gain}}$

conservation of Energy:  $\rightarrow$

$$|\Delta U_{\text{lost}}| = \Delta U_{\text{gain}}$$

$$q(V_+ - V_-) = \mathcal{E}(V_+ - V_-)$$

Rate of potential gained

$$= \frac{\Delta U_{\text{gain}}}{\Delta t} = \frac{\mathcal{E} \cdot (V_+ - V_-)}{\Delta t}$$

$$= I \cdot (V_+ - V_-) \text{ since } I = \frac{\mathcal{E}}{\Delta t}.$$

$$\text{THUS: } \frac{\Delta U_{\text{gain}}}{\Delta t} = \frac{|\Delta U_{\text{lost}}|}{\Delta t} = I \cdot \Delta V$$

$$\text{WHERE } \Delta V \equiv V_+ - V_-.$$

Note:  $I \cdot \Delta V = \left(\frac{\Delta V}{R}\right) \cdot \Delta V$   
 $= \frac{\Delta V^2}{R}$

ALSO  $I \cdot \Delta V = I \cdot (I \cdot R)$   
 $= I^2 \cdot R$

THUS, rate of heat generated in resistor =  $I^2 \cdot R = \frac{\Delta V^2}{R}$



WHERE  $\Delta V =$  BATTERY VOLTAGE and ALTERNATIVELY  $I =$  CURRENT.

NOTE:  $I \cdot \Delta V =$  POWER delivered TO CIRCUIT by BATTERY, unit is  $\frac{\text{Joules}}{\text{sec}} = \text{Watts (W)}$ .

sec 26.01 : SERIES

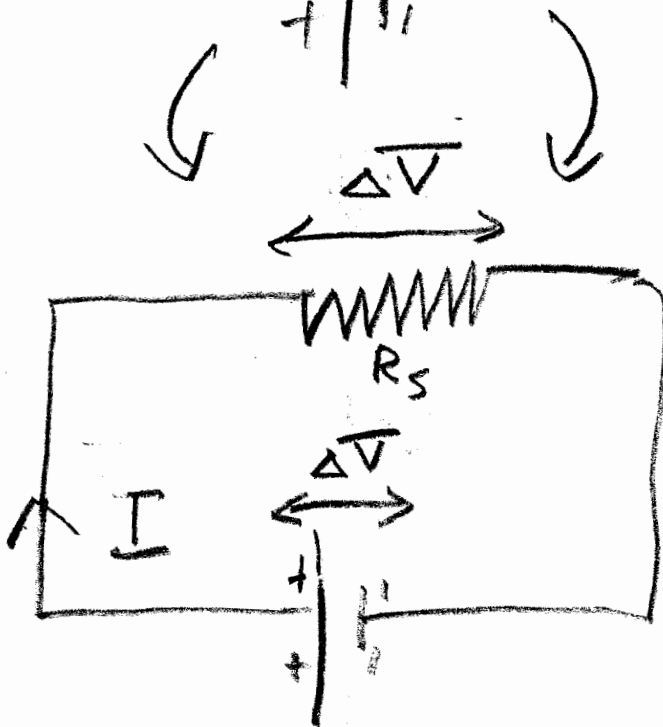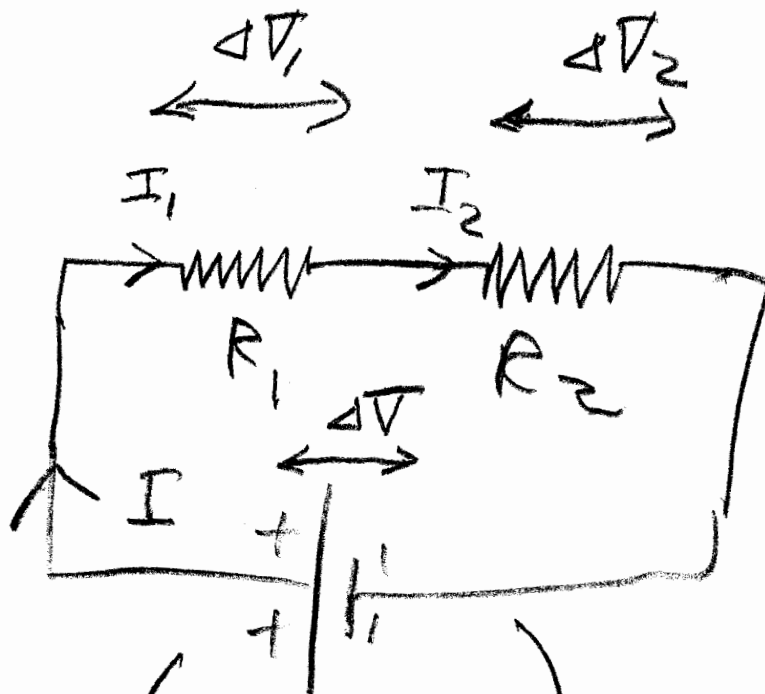(4)


$I_1 = I_2 = I$   
CONSERVATION OF CHARGE




$\Delta V = \Delta V_1 + \Delta V_2$  conservation of Energy.

$I \cdot R_s = I \cdot R_1 + I \cdot R_2 \Rightarrow R_s = R_1 + R_2$

# Sec 26.1 : parallel

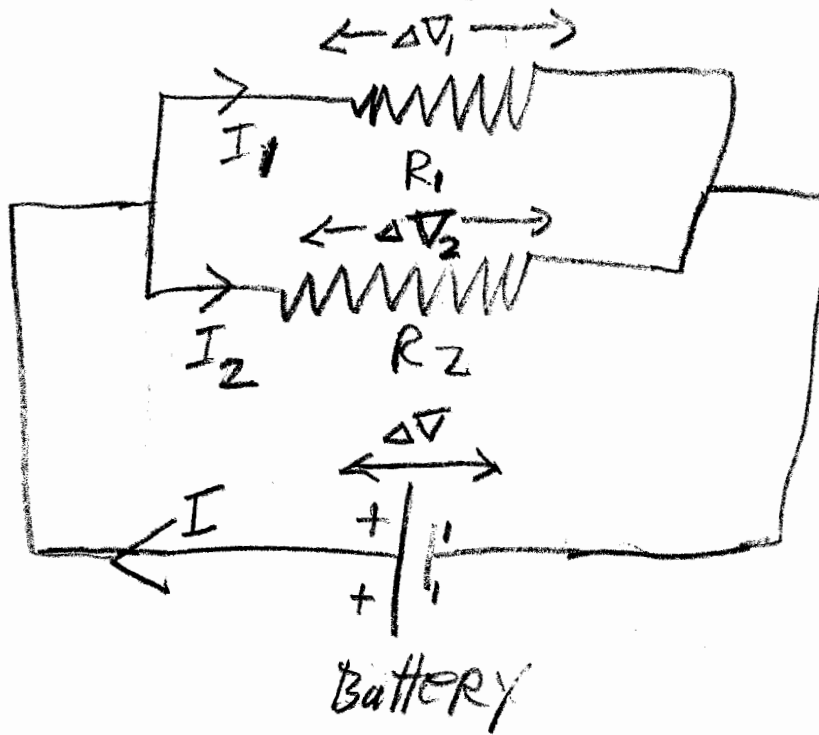

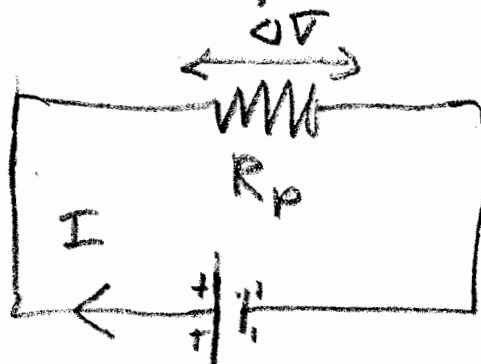$\Delta V_1 = \Delta V_2 = \Delta V$  from conservation of energy,



$$I = I_1 + I_2$$

$$\frac{\Delta V}{R_p} = \frac{\Delta V}{R_1} + \frac{\Delta V}{R_2}$$

Thus:  $\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2}$  OR  $R_p = \frac{R_1 \cdot R_2}{R_1 + R_2}$