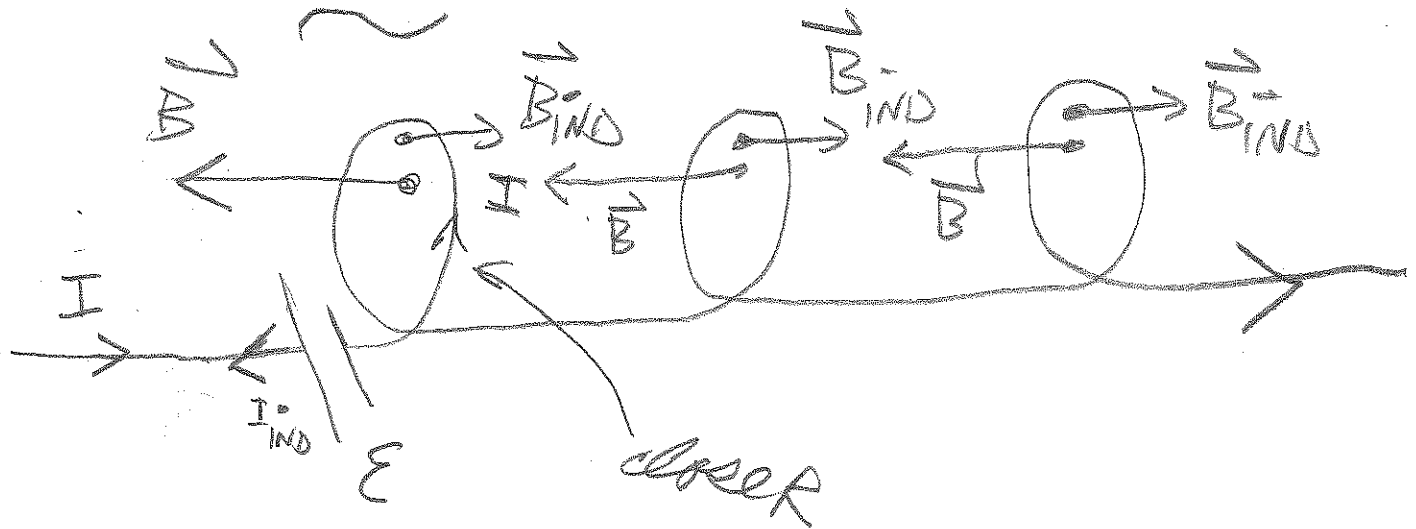


4-30-14

CH 30

Sec. 30.2



$$|\vec{B}| = B \approx \mu_0 n \cdot I$$

if  $I$  increases,  $|\vec{B}|$  increases.

$\vec{B}_{IND}$  opposes increase in  $\vec{B}$ .

$\mathcal{E}$  causes  $I_{IND}$  associated

with  $\vec{B}_{IND}$ . Net effect

on next PAGE.


4-30-14

(2)

Sec 30.2

WEB-BASED  
NARRATIVE: fig 30.6,

P996 : SELF-INDUCTANCE

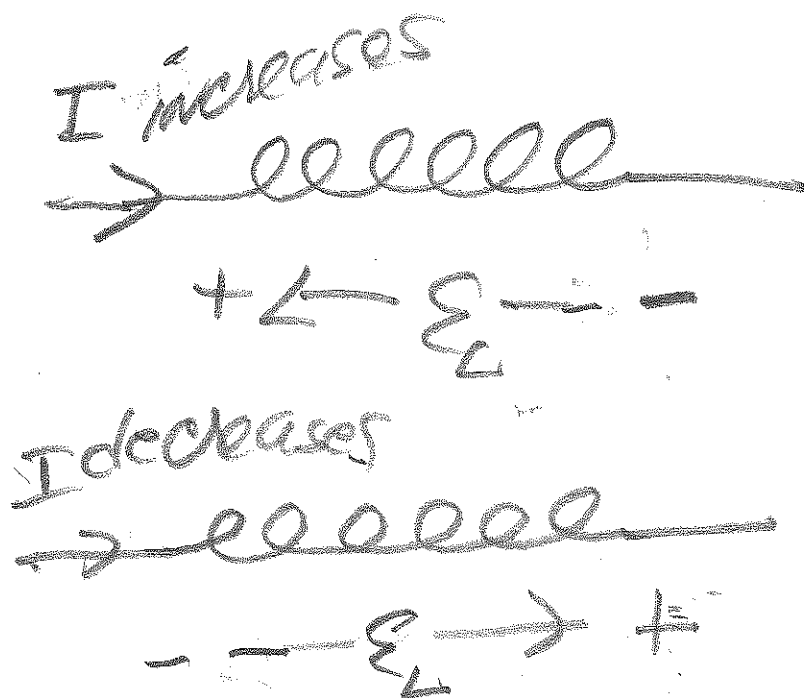

$$\epsilon_L = N \left| \frac{d\Phi_B}{dt} \right|$$

$$= L \left| \frac{dI}{dt} \right|$$


$$L = \frac{N\Phi_B}{I}$$

= inductance of solenoid.

Sec 30.3 see Eqn 30.9,

P999  $\Rightarrow U = \frac{1}{2} LI^2$


Energy

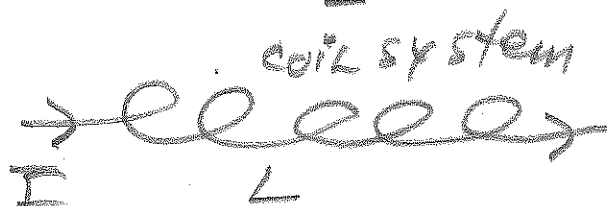


Insert: sec 30.3

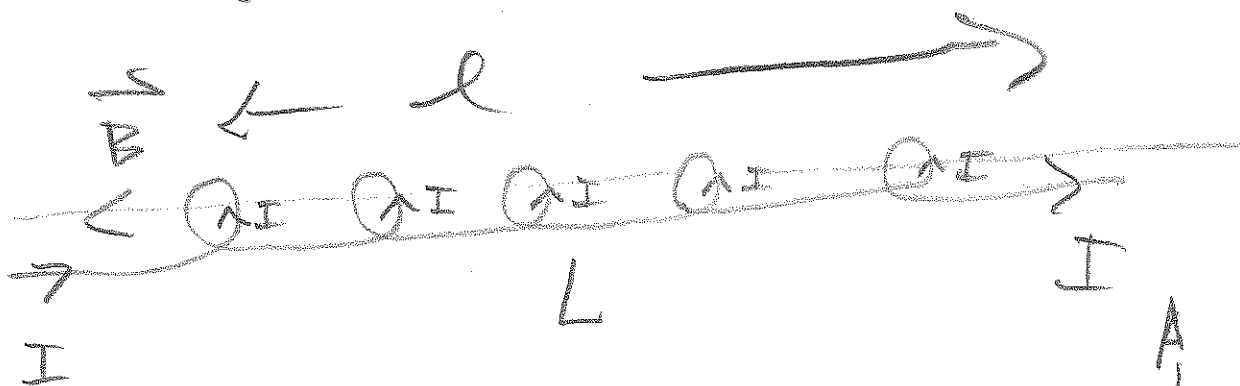(2)

Energy in system: Energy in space  
within coil.



$$U_B = \frac{1}{2} LI^2$$

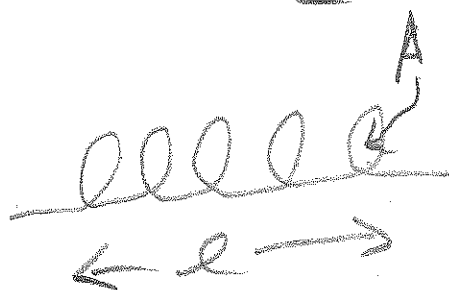

$$U_B = u_B \cdot \text{volume}, \quad u_B = \text{energy density} \left( \frac{\text{J}}{\text{m}^3} \right)$$

$$\frac{1}{2} LI^2 = u_B \cdot A \cdot l$$

see # 15, Quiz 30 (CH 30)

$$\mu L = \frac{\mu_0 AN^2}{l}$$

ALSO use:  $B = \mu_0 \frac{N}{l} I$

$$\rightarrow I = \frac{B \cdot l}{\mu_0 N} \Rightarrow u_B = \boxed{\frac{B^2}{2\mu_0} \left( \frac{\text{J}}{\text{m}^3} \right)}$$



(3)

see 30-3 :

Note:  $d\mathcal{U} = L i di$

$$\mathcal{U} = \int_0^I L i di$$

$$\mathcal{U} = \left. \frac{1}{2} L i^2 \right|_0^I = \frac{1}{2} L I^2$$

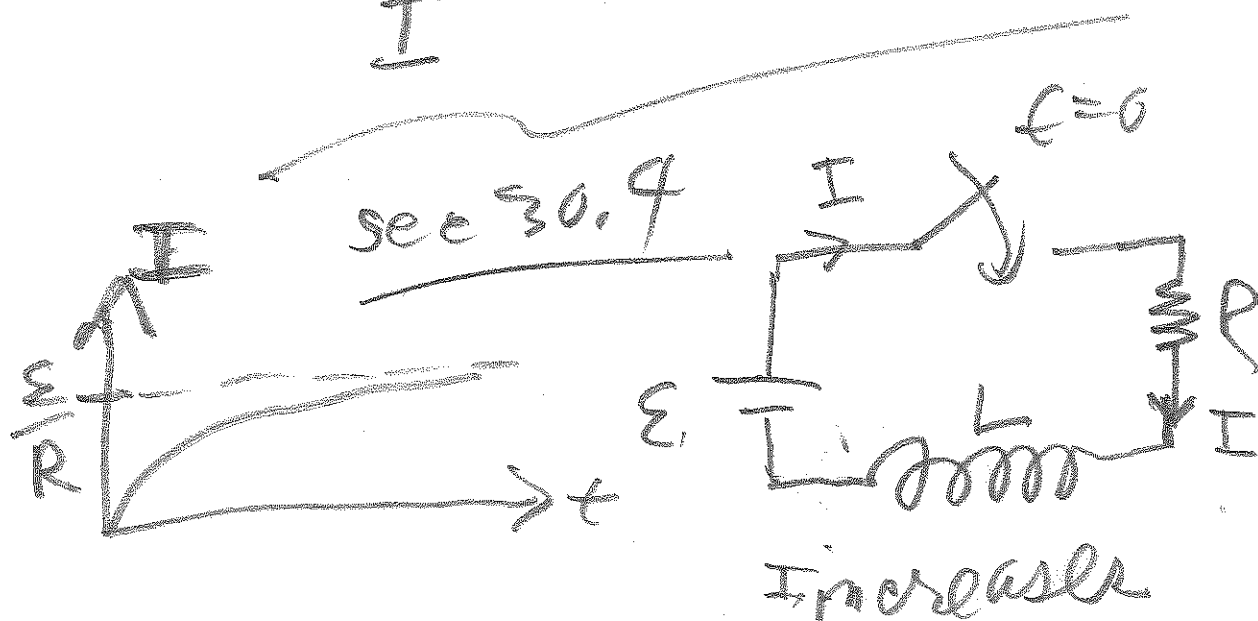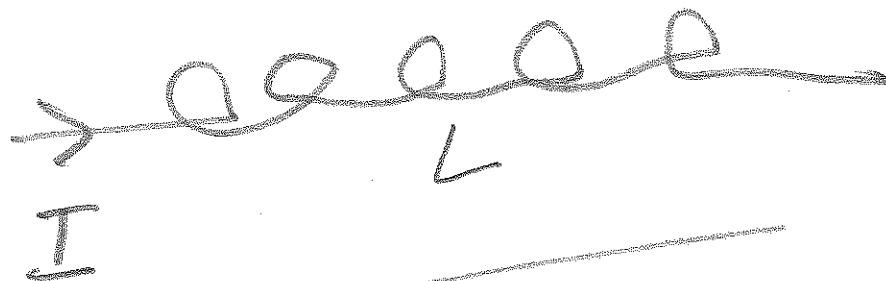

C4

Sec 30.4


$$I = \frac{\mathcal{E}}{R} (1 - e^{-t/\tau})$$

$$\tau = L/R$$

BACKTRACK: Sec 30.3

note: We derive  $L$ .

Sec. 30-5: L-C circuits.

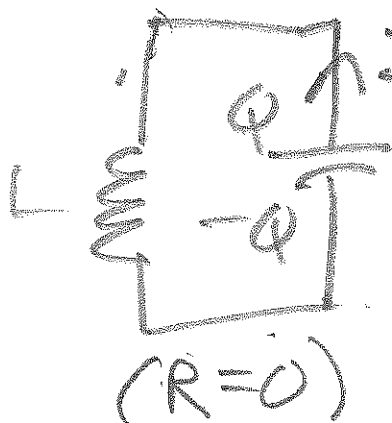

(R=0)

$$\frac{1}{2} L I^2 + \frac{Q^2}{2C} = \frac{Q_{MAX}^2}{2C}$$
$$Q = Q_{MAX} \cos(\omega t + \phi)$$
$$\omega = \frac{1}{\sqrt{LC}}$$


question from FLOOR:

(5)

where does  $I$   
come from?

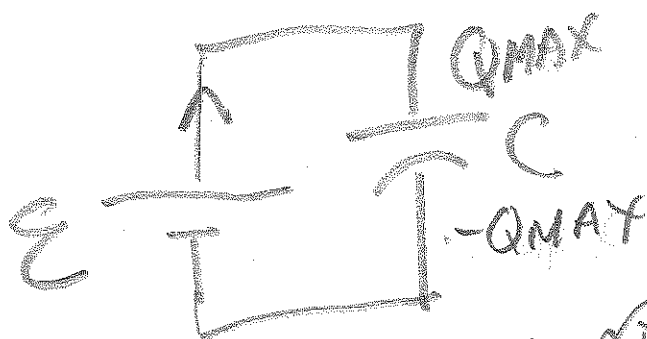Example:

step (A) CHARGE UP  
A CAPACITOR TO  
MAX CHARGE  $Q_{MAX}$



step (B): dis-connect  
CAPACITOR  $C$  FROM BATTERY

step (C): connect  $C$  TO  $L$ .

step (c.)

increases

sec  
30.5



decreases  
initially.

$$I = -\frac{dQ}{dt}$$

$\frac{dI}{dt} > 0$  initially

$Q$  decreasing

$$|\epsilon_L| = \frac{Q}{C}$$

$$|\epsilon_L| = L \frac{dI}{dt} = -L \frac{d^2Q}{dt^2}$$

$$\sum \Delta V_{loop} = 0 = \frac{Q}{C} - L \frac{dI}{dt}$$

$$\Rightarrow L \frac{dI}{dt} = \frac{Q}{C}$$

$$-L \frac{d^2Q}{dt^2} = \frac{Q}{C} \rightarrow L \frac{d^2Q}{dt^2} = -\frac{Q}{C}$$

(7)

solution:  $Q = Q_{\text{max}} \cos(\omega t + \phi)$

$$\omega = \frac{1}{\sqrt{LC}}$$


In this case:  $\phi = 0$

since  $I = 0$  at

$$t = 0,$$

see 30.5

$$Q = Q_{\text{max}} \cos \omega t$$

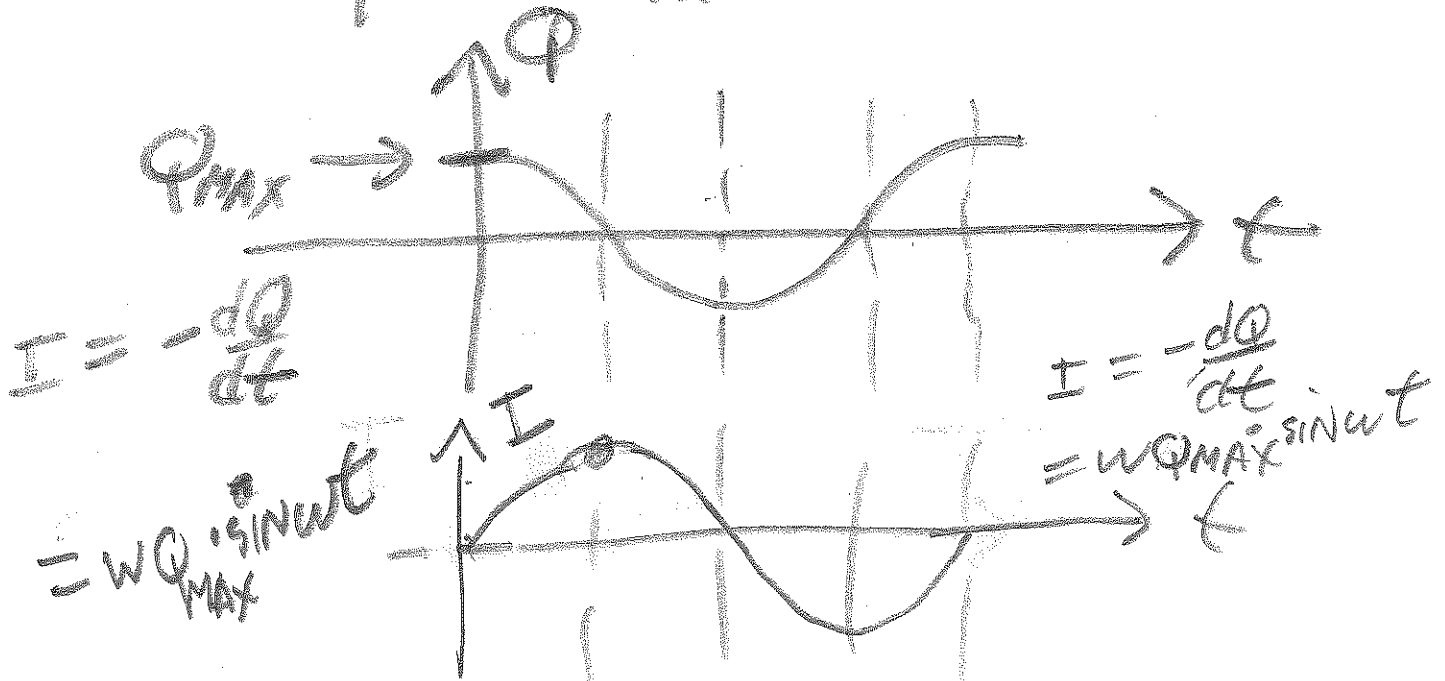



ch 30-44

$$\text{ch 30 } \frac{1}{2} LI^2 + \frac{1}{2} \frac{Q^2}{C} = \frac{1}{2} \frac{Q_{\text{MAX}}^2}{C} \quad (8)$$

FOR ALL TIME:

$$\text{p44 } \frac{1}{2} mV^2 + \frac{1}{2} kx^2 = \frac{1}{2} kA^2$$

4A-analogy