

4B 5-12-14 Part 2

LINK: 3-28-14 (date of NOTES)

supplement:


ch 7 $\frac{1}{2} kx^2 + \frac{1}{2} mv^2 = \frac{1}{2} kA^2$

ch 30 $\frac{Q^2}{2C} + \frac{1}{2} LI^2 = \frac{Q_{MAX}^2}{2C}$
 → AC circuits

ch 29 QUIZ 29

CAR STARTER

EXAMPLE

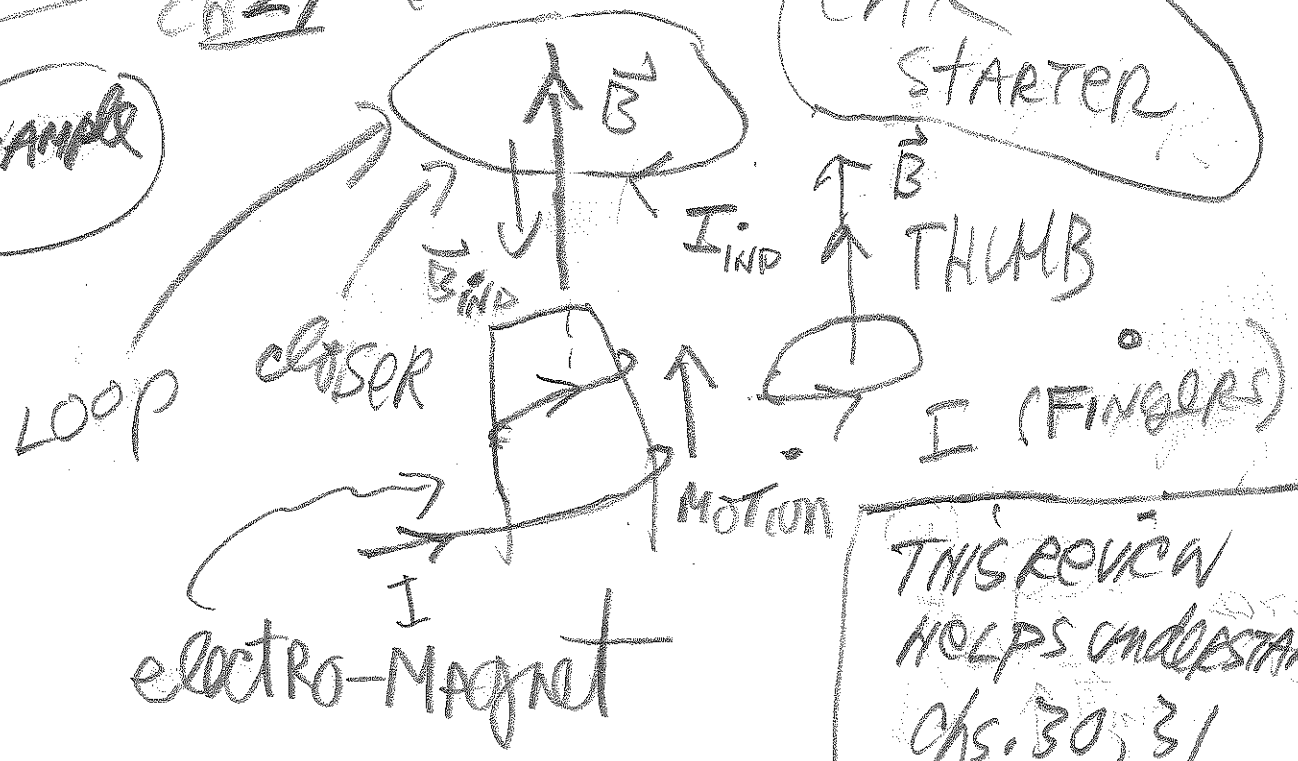


THIS REVIEW HELPS UNDERSTAND CHS. 30, 31

after BREAK


Explain RLC circuit
from 'bottom up.'

analyze it.

$$\epsilon = V \cos \omega t$$

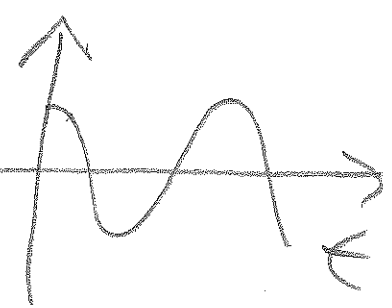

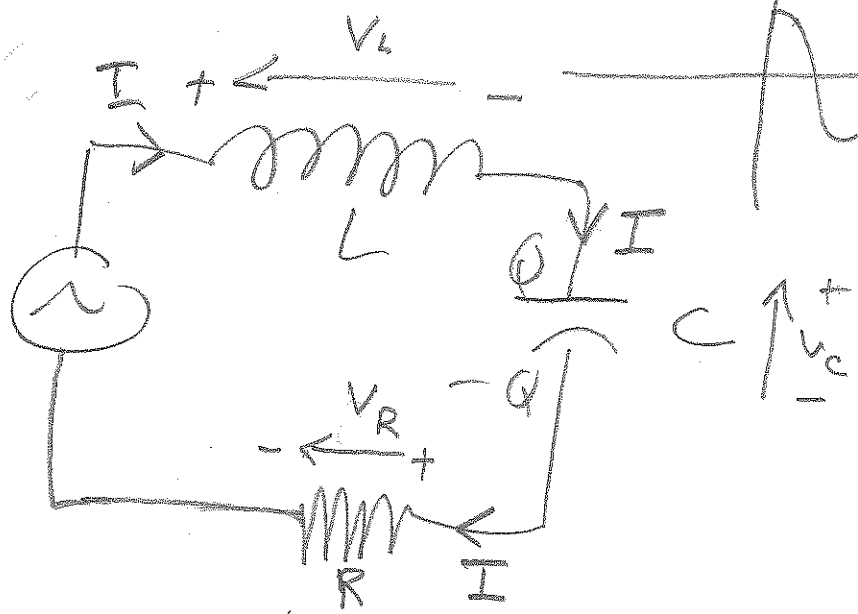$V \cos \omega t = \epsilon$
"PUSH"
at ω .




LOOK at each component.
NOTES:

- (A) V_R and I ARE IN PHASE
- (B) I LAGS V_L (90°)
- (C) I LEADS V_C (90°)

Sec 31.2

(A) R alone:

$$I = \frac{V}{R} \cos \omega t$$

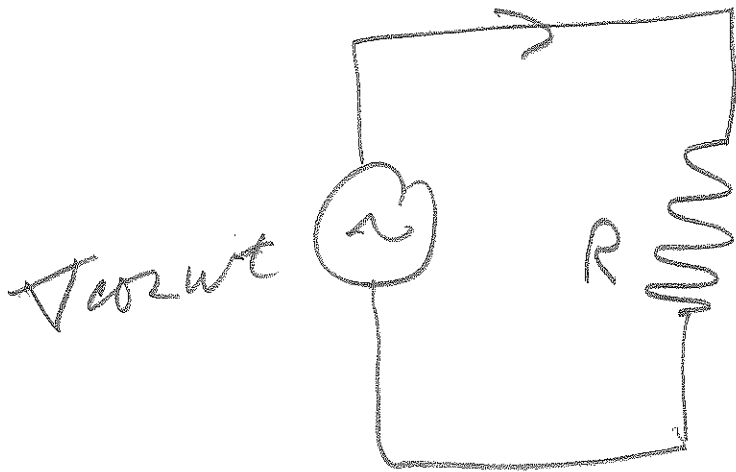

$$+ \uparrow V_R \equiv V_+ - V_-$$


$$V_R = I \cdot R$$

Ohm's Law $I = \frac{V_R}{R}$ CW 19



note: $V_R \doteq V \cos \omega t \Rightarrow I = \boxed{\frac{V}{R} \cos \omega t}$

$$\sum_{\text{Loop}} \Delta V = 0$$

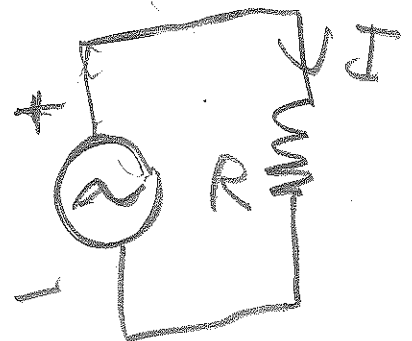
$$\sum_{\text{Loop}} \Delta V = V \cos \omega t - V_R = 0$$



(10)

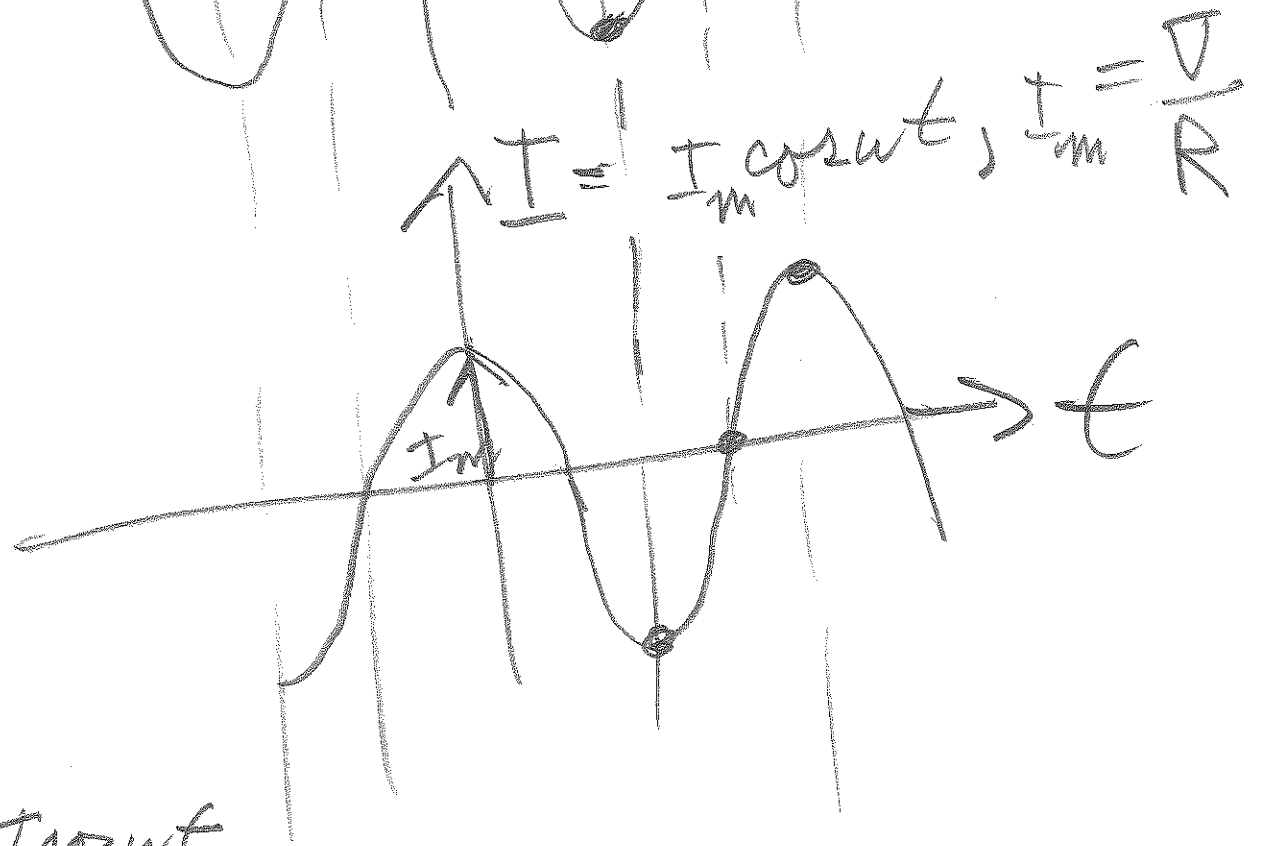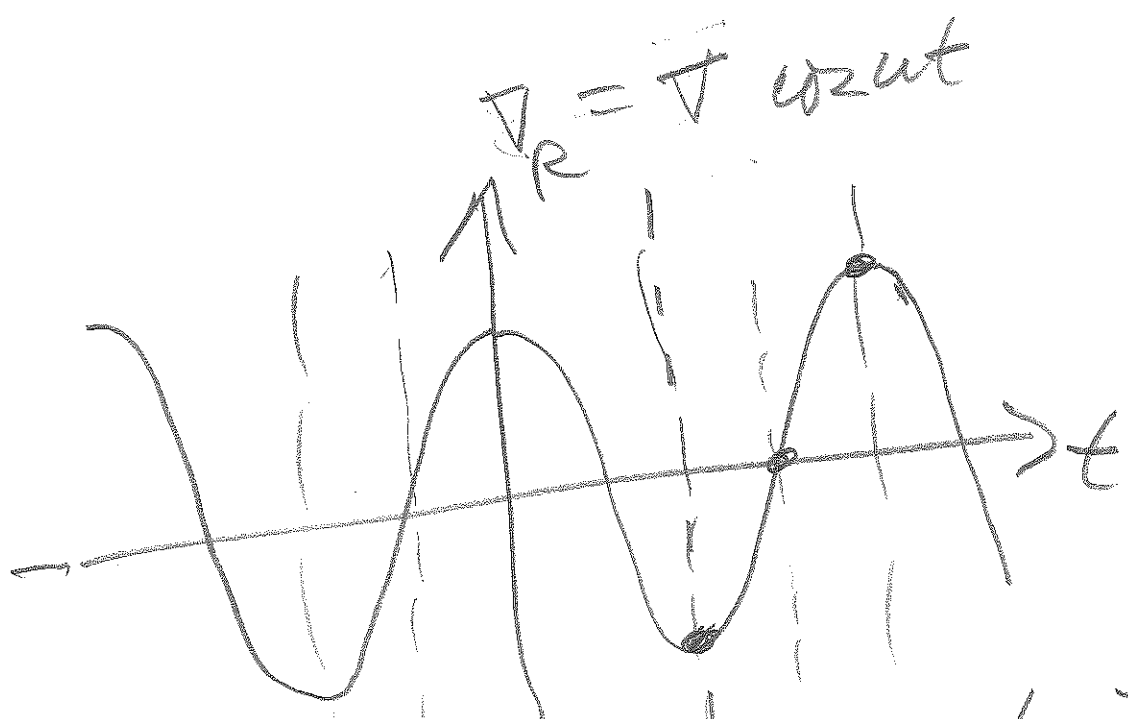

$\mathcal{E} = V \cos \omega t$


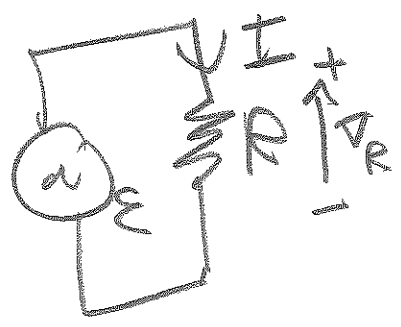


I and V_R are in phase

sec 31.2

CV




(B) L-alone:

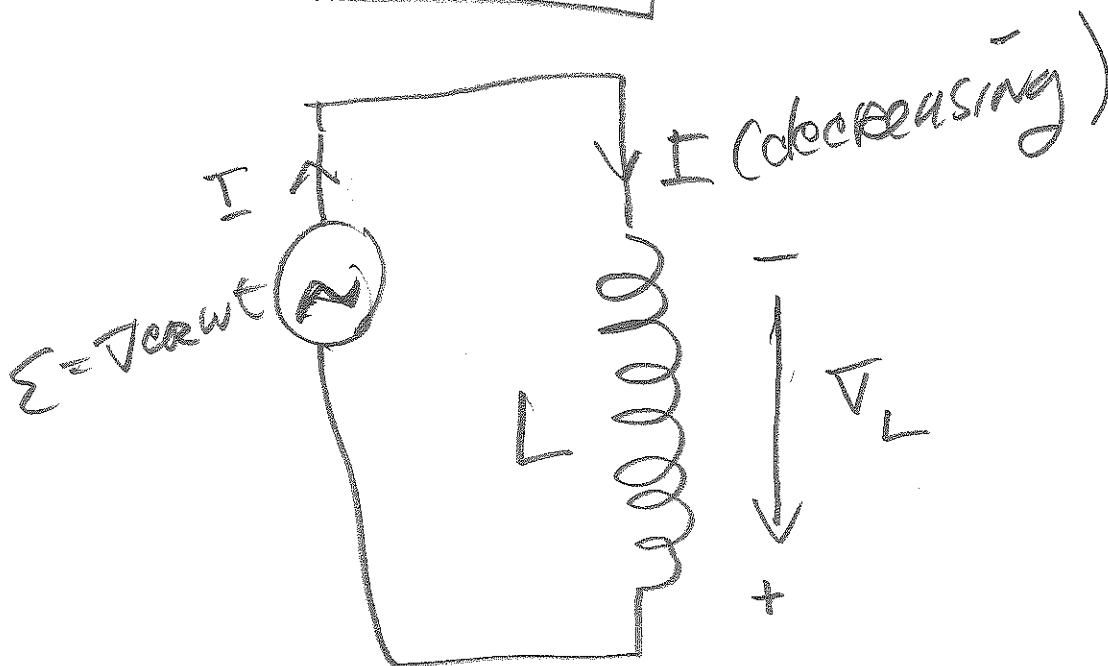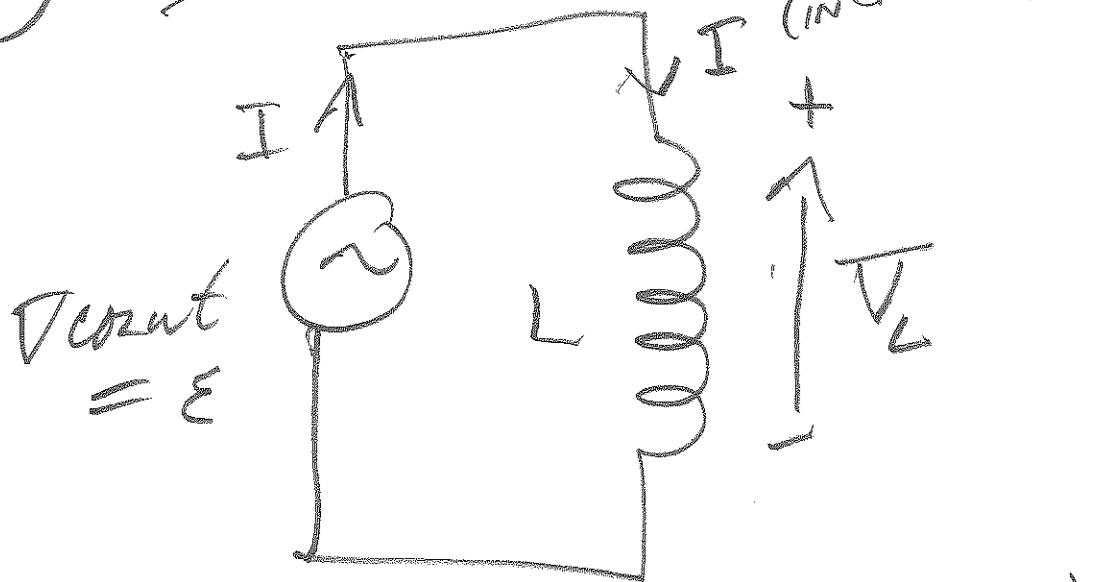

$$\mathcal{E} = \nabla_L = \nabla \cos \omega t \iff \sum \Delta \nabla = 0 \quad (12)$$

$$\nabla \cos \omega t - \nabla_L = 0$$

$$\nabla_L = \nabla \cos \omega t$$

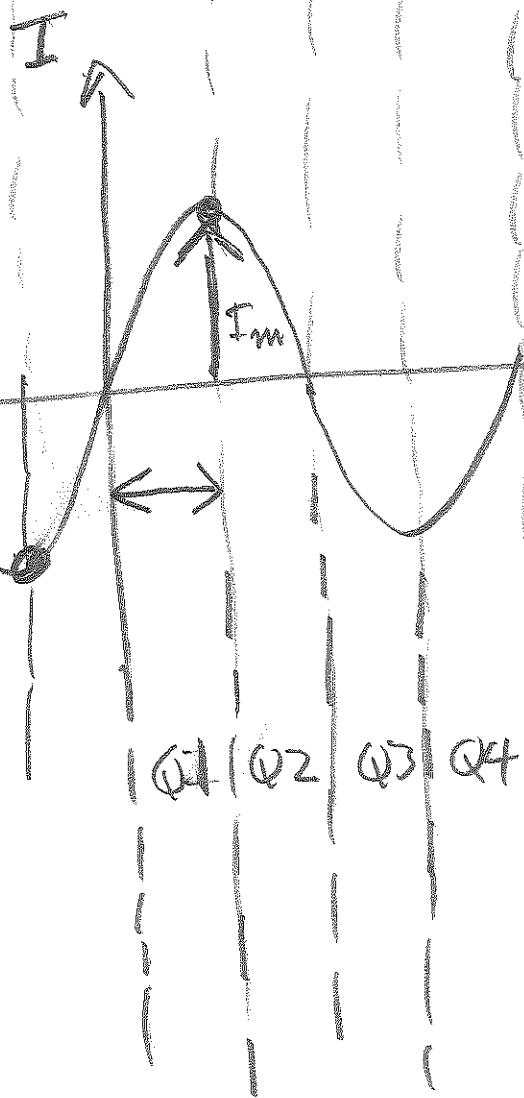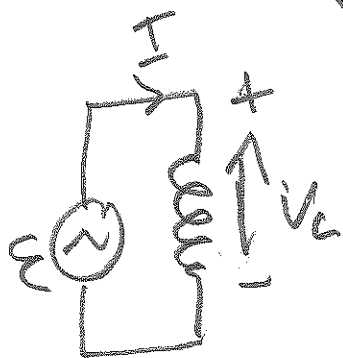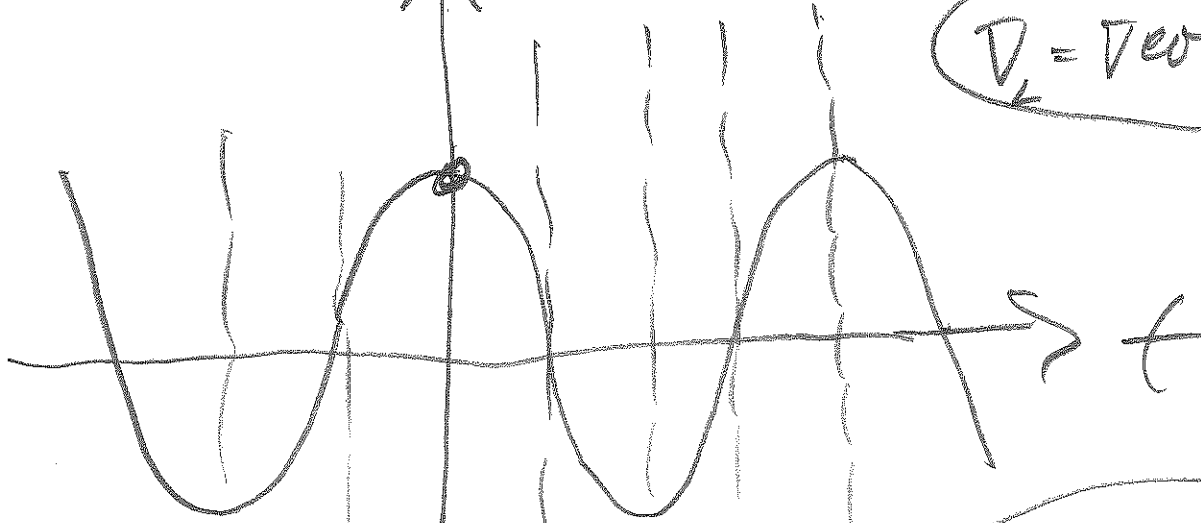

I LAGS ∇_L
by $90^\circ = \frac{\pi}{2}$

$$I = I_m \sin \omega t$$

$$I = I_m = \frac{\nabla}{\omega L}$$



$$I = I_m \sin \omega t$$

$$= I_m \cos(\omega t - \frac{\pi}{2})$$

I LAGS ∇_L

ϕ_2	ϕ_1
ϕ_3	ϕ_4

(C) C-alone:

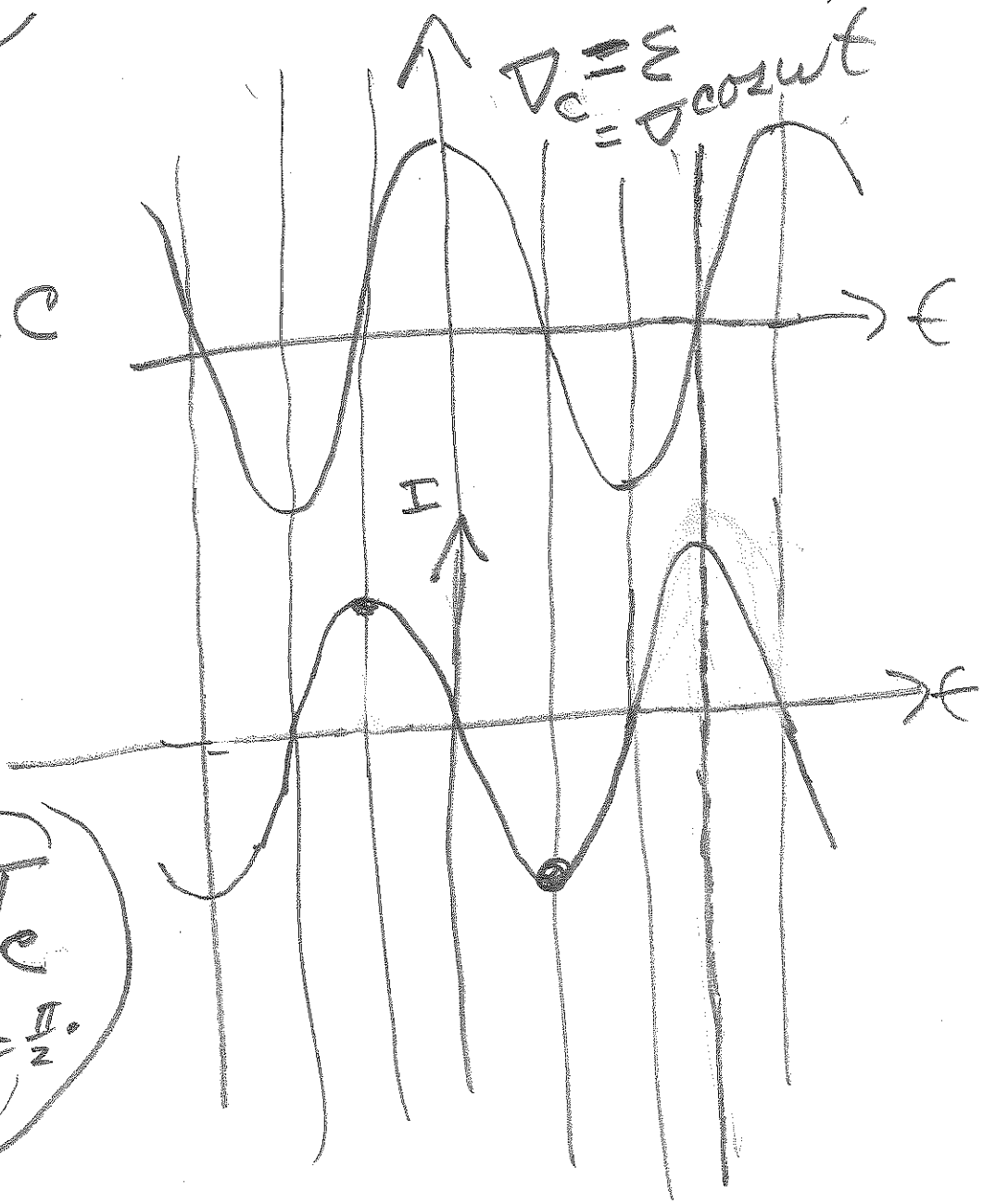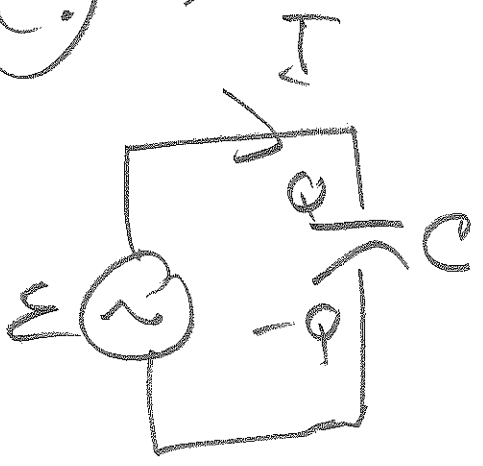

I leads V_c
by $90^\circ = \frac{\pi}{2}$.

$$I = I_m \sin \omega t$$

$$= I_m \cos \left(\omega t + \frac{\pi}{2} \right)$$

I leads V_c .

Ch 29 Notes

CHANGING flux via
CHANGING \vec{B} OR CHANGING
area A .


I. CHANGING \vec{B} :

$$|\mathcal{E}| =$$

$$\frac{\Delta \Phi_B}{\Delta t}$$

$$= A \frac{\Delta B}{\Delta t}$$

MOTION

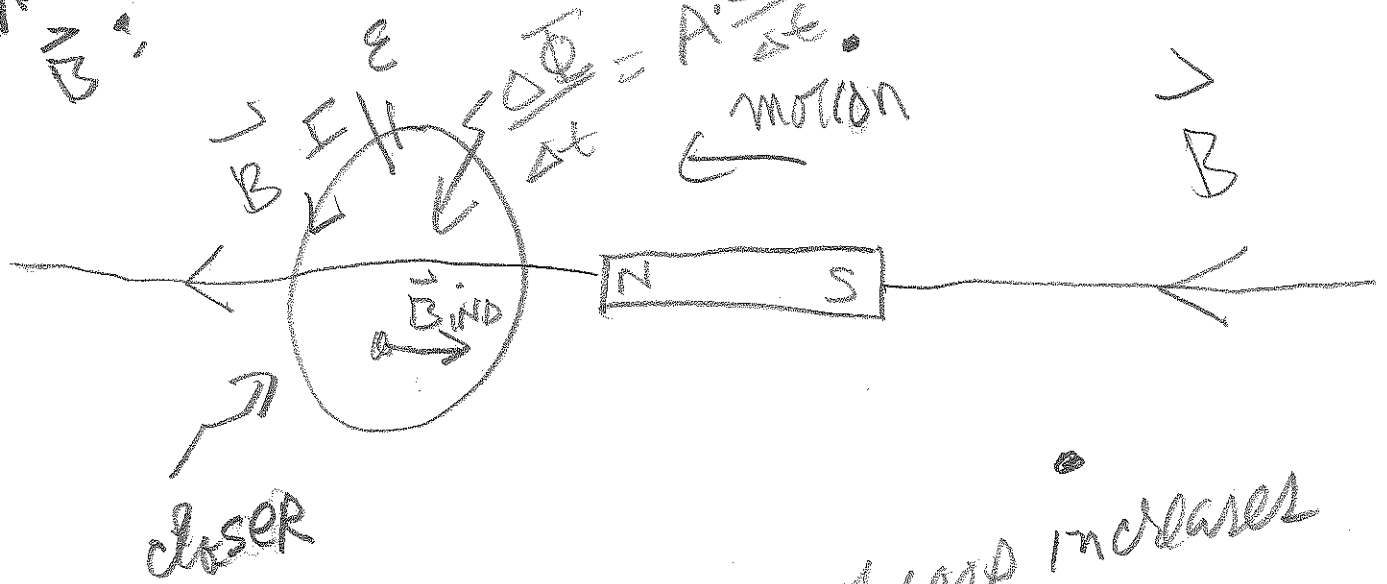


II. CHANGING area:

area increasing

$\vec{B} = \text{constant}$

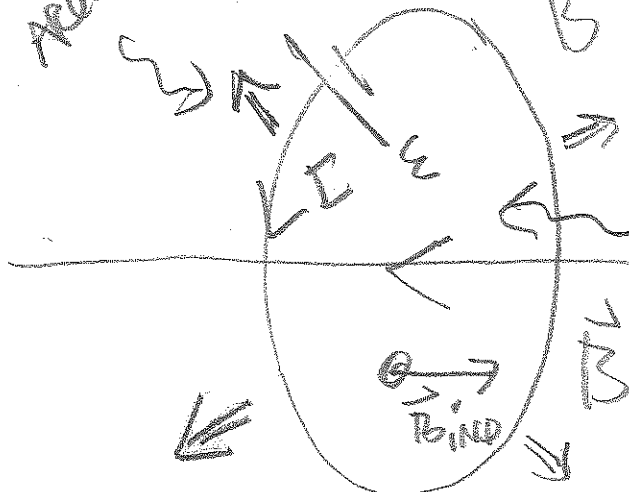
$$\frac{\Delta \Phi_B}{\Delta t} = B \frac{\Delta A}{\Delta t}$$




area of loop increases in time.

Finish ch 31,
RLC circuits!

4-4-14

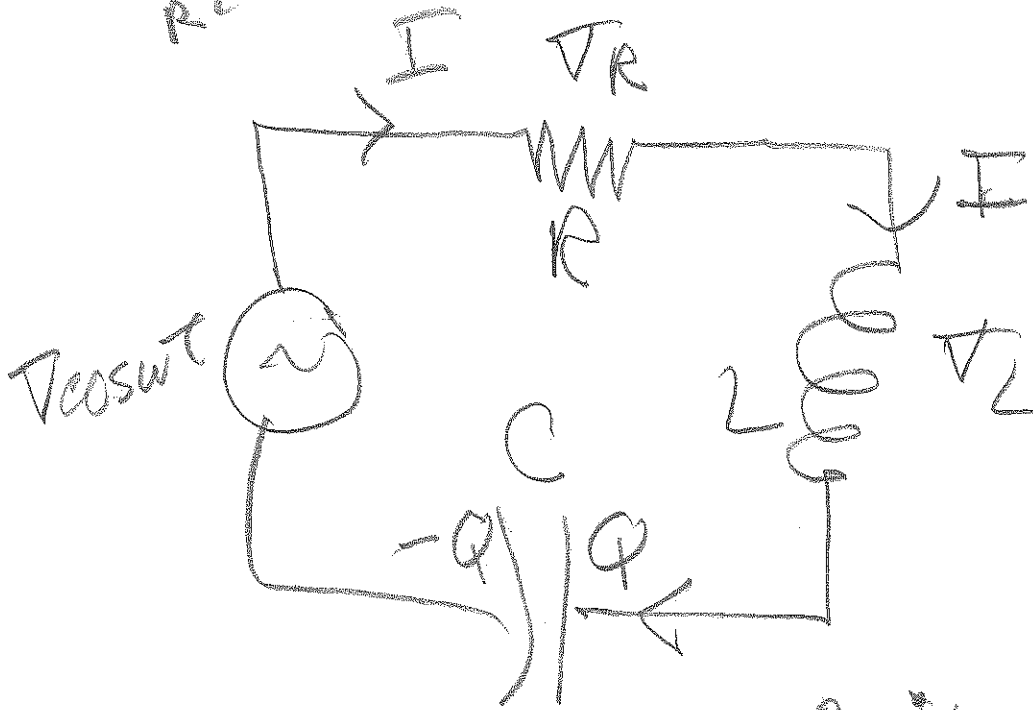


PHASOR
DIAGRAM

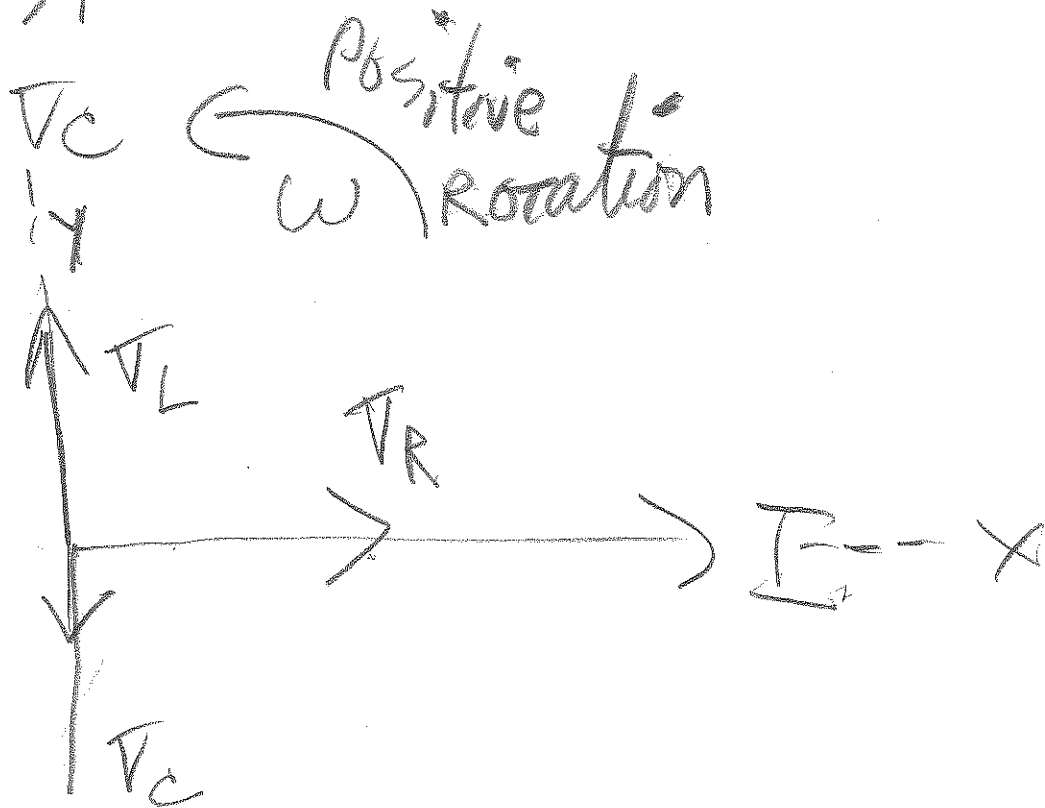

Ch 31


rewrite!

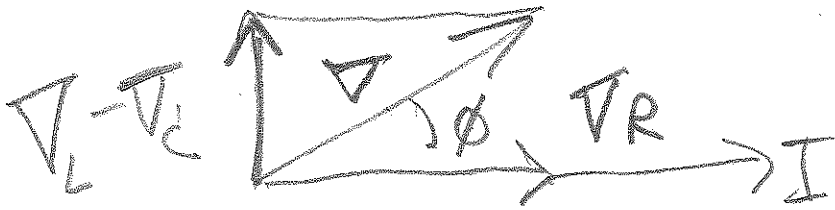

PYTHAGOREAN

THEOREM:

$$V^2 = (V_L - V_C)^2 + V_R^2$$

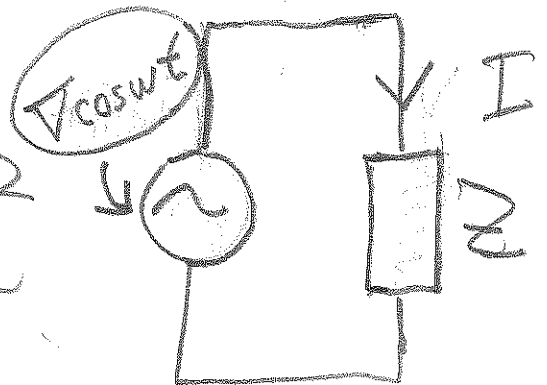

use:

$$I = \frac{V_L}{\omega L}$$

$$I = \frac{V_C}{\frac{1}{\omega C}}$$

$$I = \frac{V_R}{R} \quad \text{OHM'S LAW}$$

$$(I \cdot Z)^2 = \left(I \cdot \omega L - I \cdot \frac{1}{\omega C} \right)^2 + I^2 R^2$$

$$Z = \sqrt{\left(\omega L - \frac{1}{\omega C} \right)^2 + R^2}$$

$$I = \frac{V}{Z} = \frac{V}{\sqrt{\left(\omega L - \frac{1}{\omega C} \right)^2 + R^2}}$$

Larger than
static background of
radio receiver.

