

5-2-14 CH 3 / Part 3


Practice problem.

practice

ALWAYS START OFF:

$$\omega_{res} = \frac{1}{\sqrt{LC}}$$
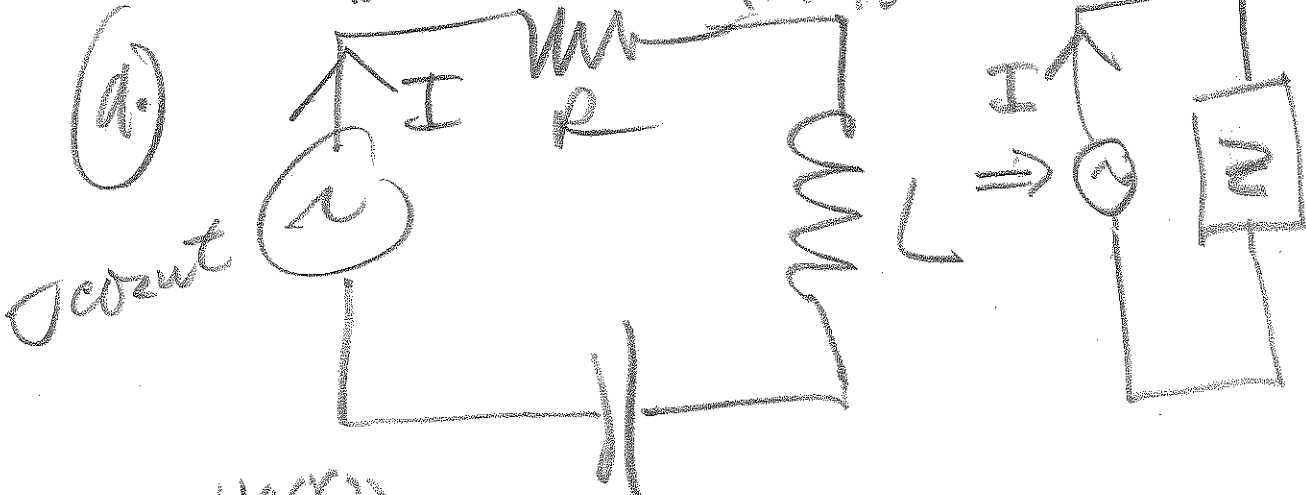
$$\frac{1}{\sqrt{0.900 \cdot 2 \times 10^{-6}}} = \frac{1}{\sqrt{1.8 \times 10^{-6}}} = 745 \frac{\text{RAD}}{\text{s}}$$



current

DO FIRST $\omega = 1000$
 $\rightarrow 750$ RAD/s
 500 C

$$500 < \omega_{res} < 750 \quad Z = \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}$$

$$R = 200 \Omega, L = 0.900 \text{ H}$$

$$C = 2 \times 10^{-6} \text{ F}$$

$$Z = \sqrt{(200)^2 + (750 \cdot 0.9 - \frac{1}{750 \cdot 2 \times 10^{-6}})^2}$$

table

ω (RAD/s)	Z	$WL - \frac{1}{WC}$	WORK (Ω) ²
(KMEI) 1000	447 Ω	900 Ω	$\sqrt{40000 + 160000}$
(KPFAS) 750 NEAR RESONANCE	200.2 Ω NEAR R	9 Ω	$\sqrt{40000 + 81}$
(KQED) 500	585 Ω	-550 Ω	$\sqrt{90000 + 302500}$

$R^2 = 40,000 \Omega^2$

observations:

- * NEAR RESONANCE $Z \approx R$.
- * AT RESONANCE $Z = R$.
- * SMALL R MEANS LARGE I_m

NEAR RESONANCE

(3)

$$\rightarrow \text{CHECK} = 750 \cdot 0.9 - \frac{1}{750 \cdot 2 \times 10^{-6}}$$

$$= 675 - (0.666) \times 10^3$$

$$= 675 - 666$$

$$\approx 9 \Omega$$

NEAR RESONANCE:

$$\frac{9}{670.5} \times 10^0 = 1.3\%$$



$$WL - \frac{L}{WC} \text{ for: (a) } \omega = 1000 \frac{\text{RAD}}{\text{S}}$$

$$1000 \cdot 0.9 - \frac{1}{1000 \cdot 2 \times 10^{-6}} = 900 - 500 = 400 \Omega \gg 9 \Omega$$




$$(b) \omega = 500 \frac{\text{RAD}}{\text{S}} \Rightarrow 500 \cdot 0.9 - \frac{1}{500 \cdot 2 \times 10^{-6}}$$

$$= 450 - 1000 = -550 \Omega$$

(b)	V_m	$I_m = \frac{V_m}{Z}$	WORK: $I_m = \frac{V_m}{Z}$
	1000	$(0.002) \cdot V_m$	$\frac{V_m}{447} \leftrightarrow \frac{1}{447} = 0.002$
$W_{res} \approx 750$ NEAR RESONANCE		$(0.005) \cdot V_m$ $\approx V_m/R$	$\frac{V_m}{200.2} \rightarrow \frac{1}{200.2} = 0.005$
	500	$(0.002) \cdot V_m$	$\frac{V_m}{585} \rightarrow \frac{1}{585} = 0.002$

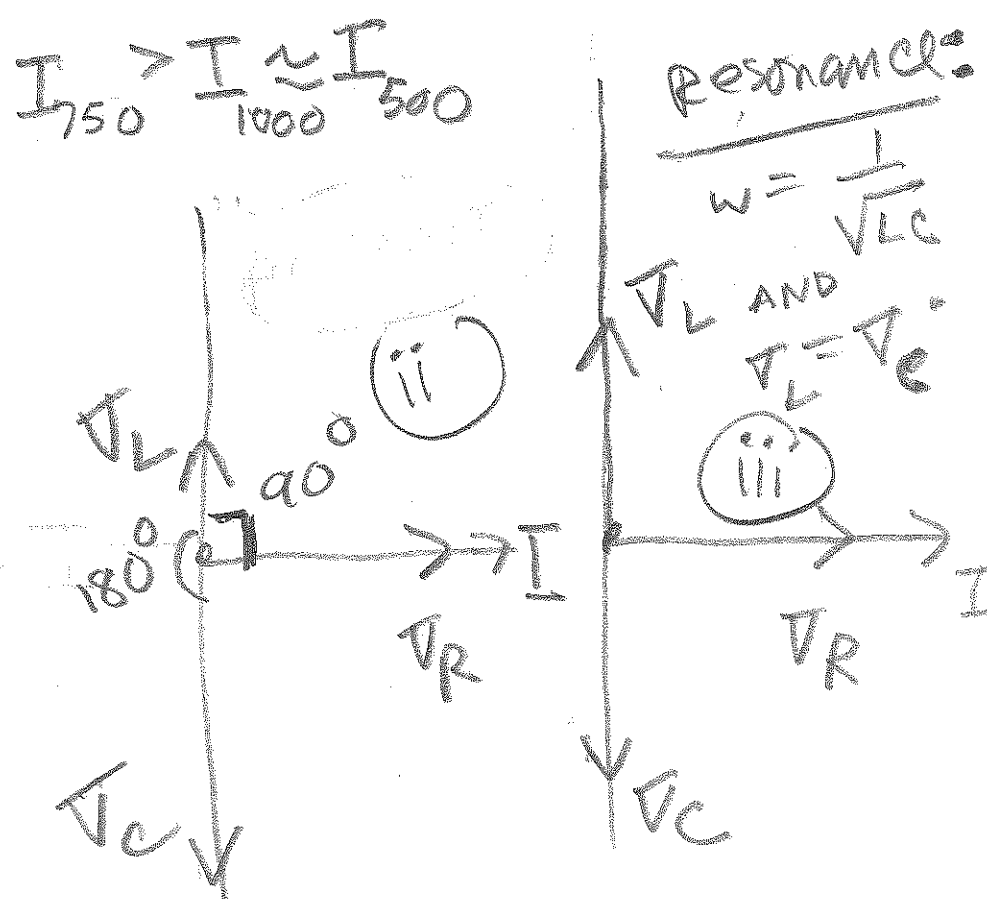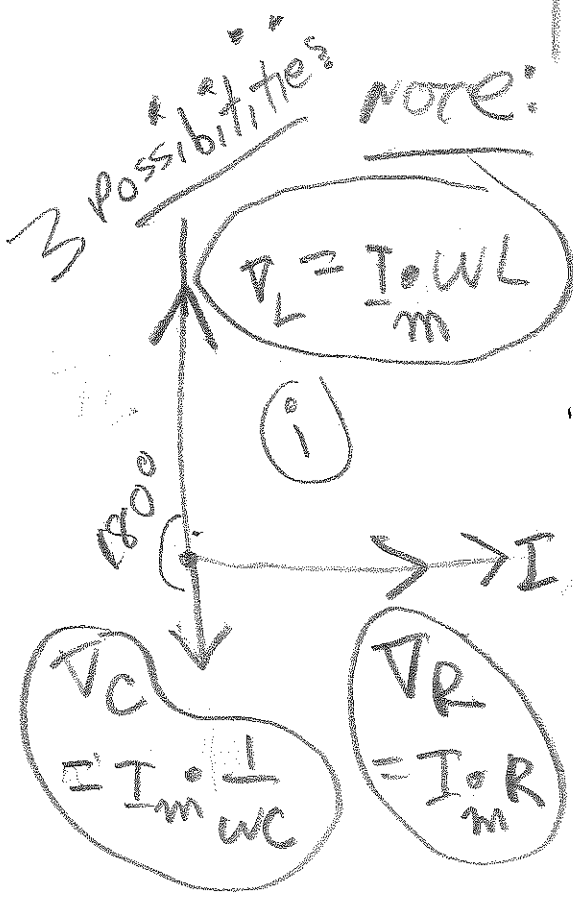

(6)

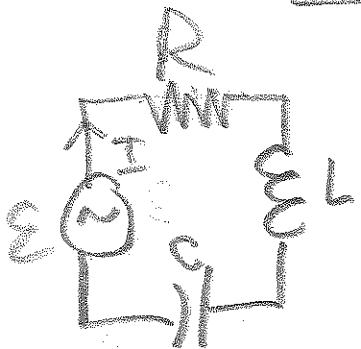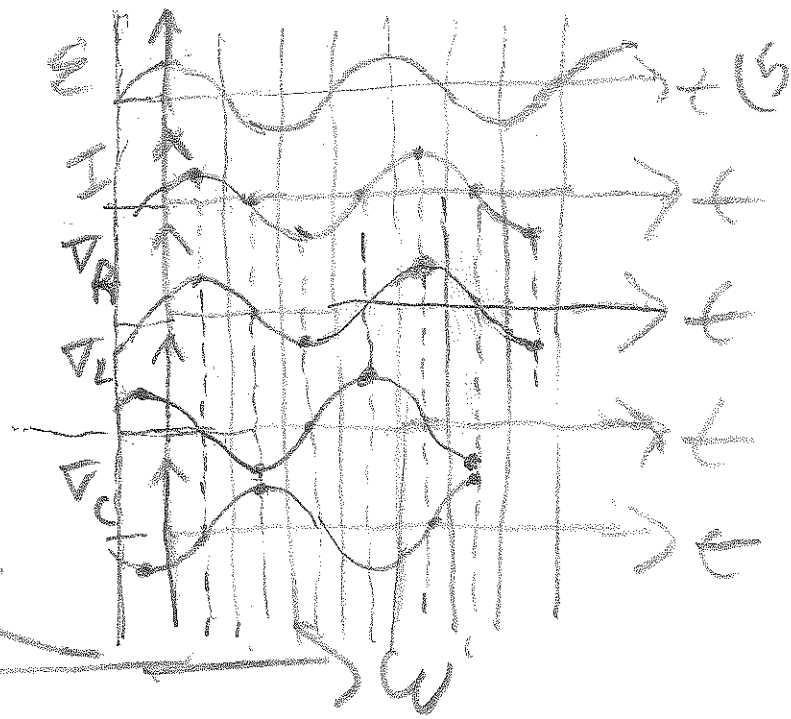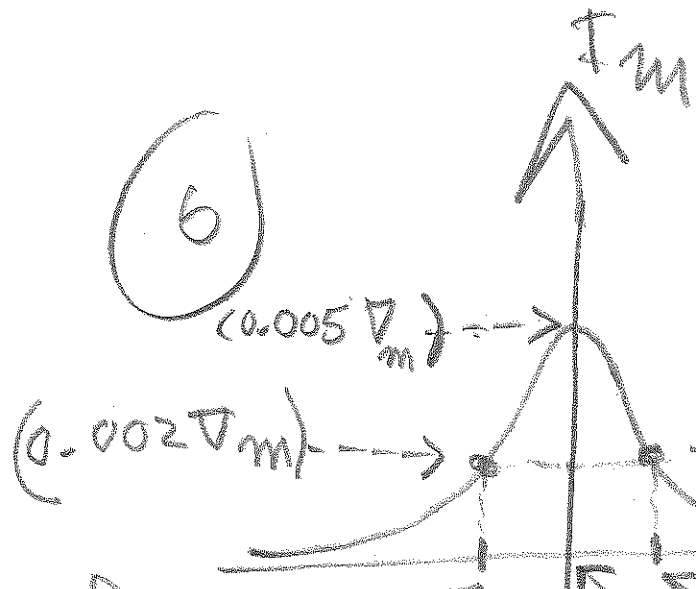

$\omega_{RES} = 745 \approx 750$

$$I_m = \frac{V_m}{Z}, \quad V_m = V$$

as in $\epsilon = V \cdot \cos \omega t$

$$I = I_m \cdot \cos(\omega t - \phi)$$

$\phi =$ complicated function of ω, L, C and R .


see notes below

(c)

$$\phi > 0^\circ$$


since $1000 > 745$

$\omega_{RES} \approx 745$

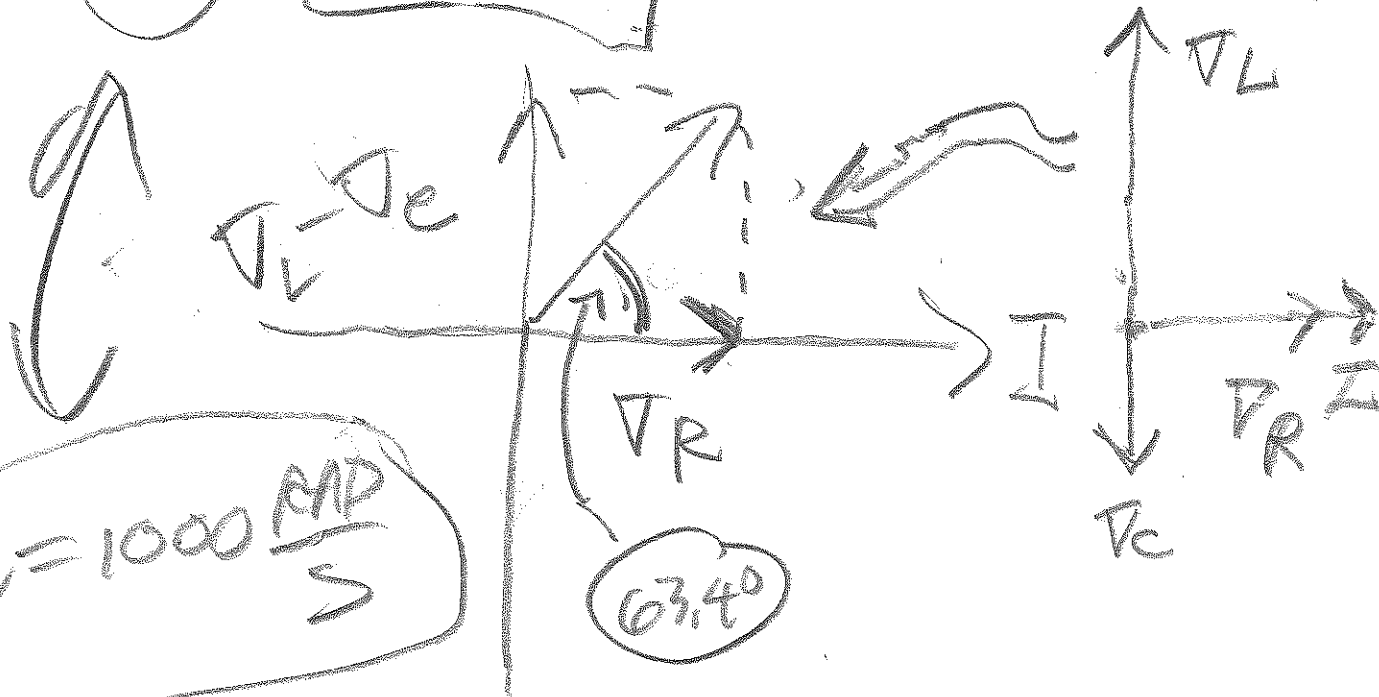

$$\omega = 1000 \frac{\text{RAD}}{\text{S}}$$

general diagrams:

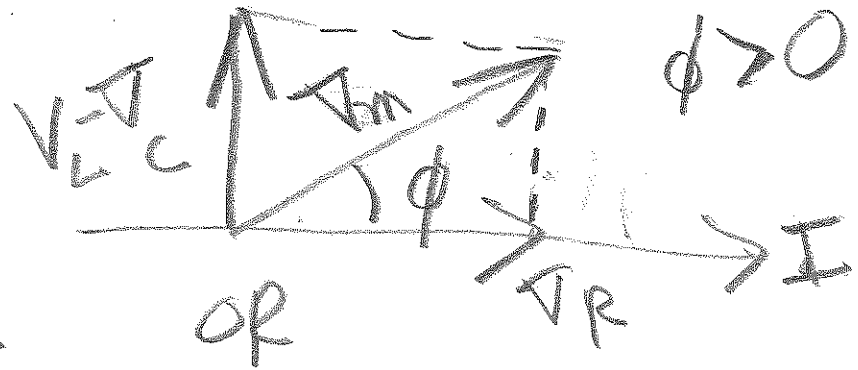


$\tan \phi =$

$$\frac{V_L - V_C}{V_R}$$



OR

$$\frac{\omega L - 1/\omega C}{R}$$

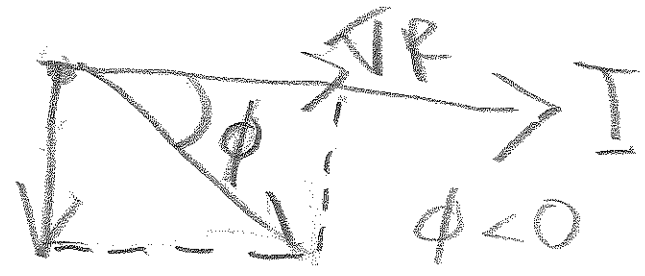

$\phi < 0$

(d)

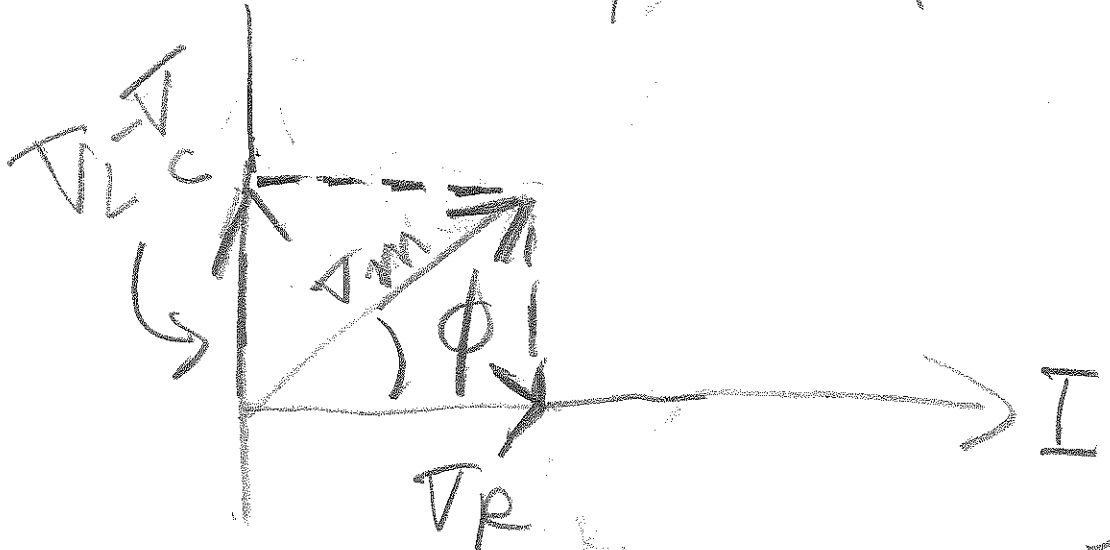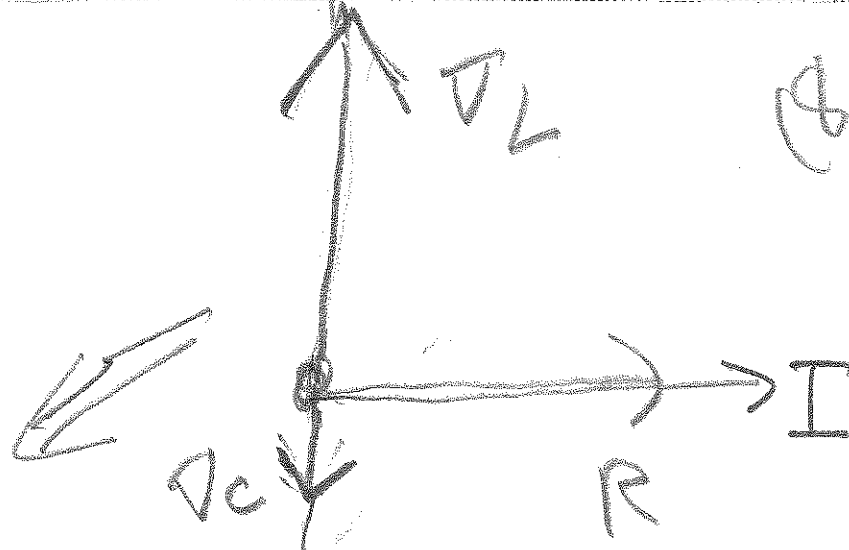

MAKE
a scale
DIAGRAM
using values of
 ω R and C .

$$\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2} = 447 \Omega$$

$$\omega L - \frac{1}{\omega C} = 400 \Omega$$

USE GRAPH
PAPER

$\omega = 1000 \text{ RAD/S}$

$R = 200 \Omega$

SKETCH ϕ .